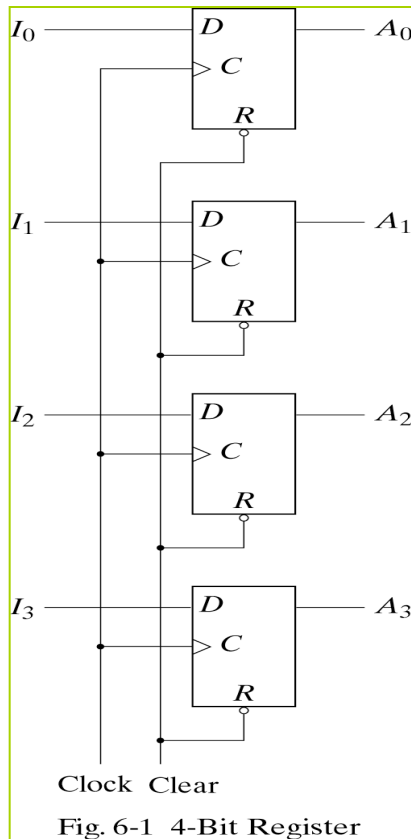


6. Registers, Counters and Memory


6.1 REGISTERS

Register- a group of binary cells suitable for holding binary information.



- ❑ Clock=1 ;input information transferred
- ❑ Clock=0 ;unchanged
- ❑ Clear=0 ;clearing the register to all 0's prior to its clocked operation.

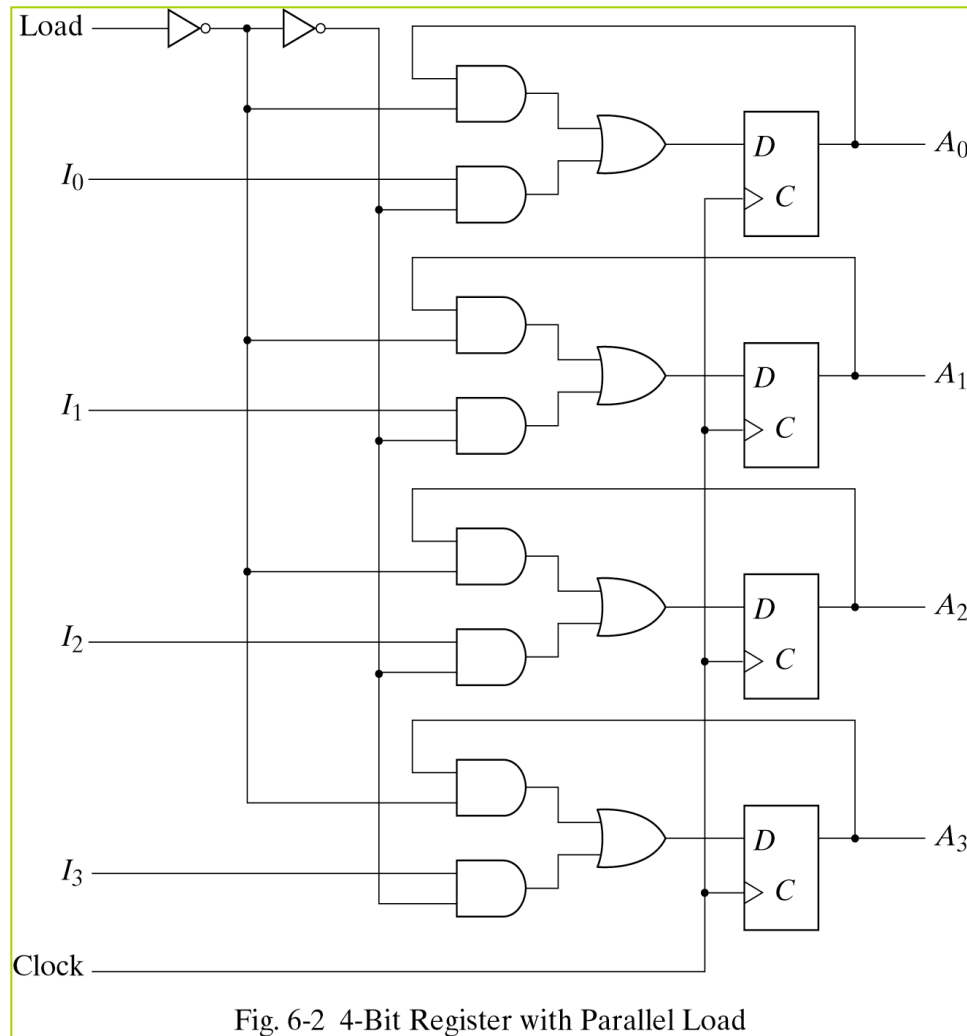
6.1 REGISTERS - Register with Parallel Load



- ❑ Clock=1 ;input information
->loading
- ❑ Clock=0 ;the content of the register ->unchanged
- ❑ Load input=1 ; the I inputs are transferred into the register
- ❑ Load input=0 ; maintain the content of the register

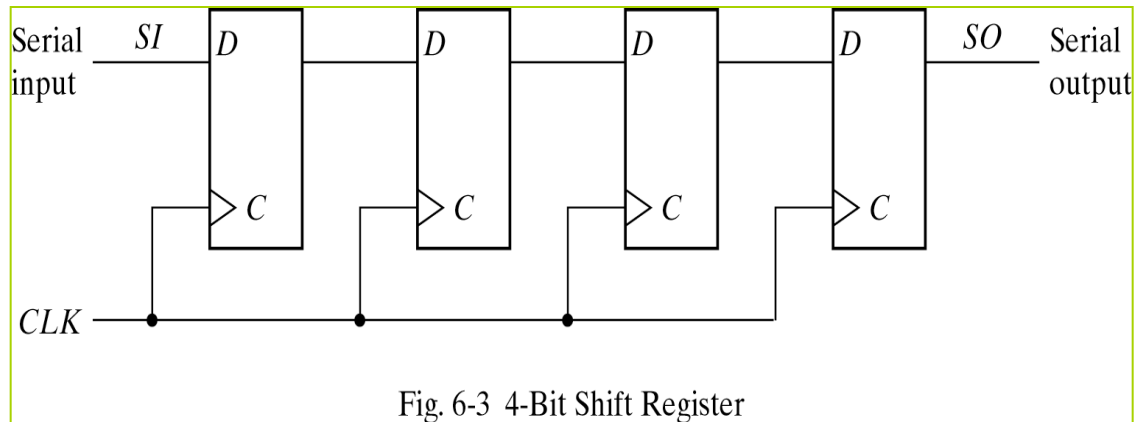
6.2 SHIFT REGISTERS

Shift register-capable of shifting its binary information in one or both directions



The simplest shift register

6.2 SHIFT REGISTERS - Serial Transfer

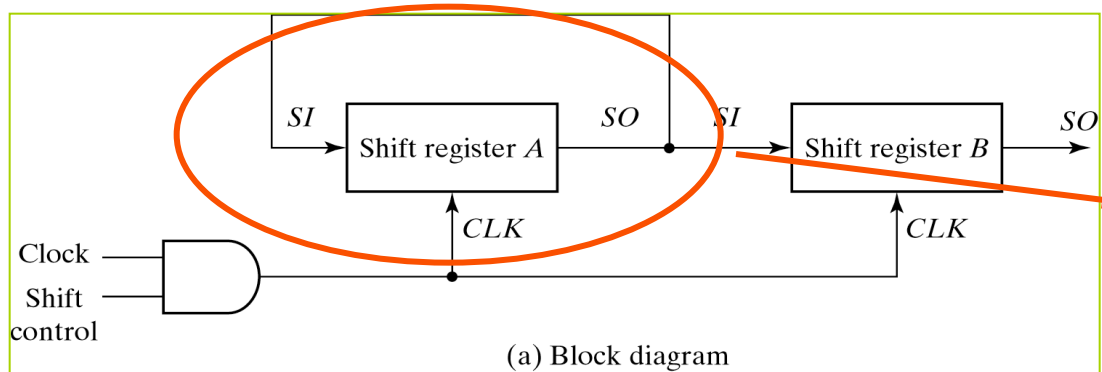

To prevent the loss of information stored in the source register

 



Fig. 6-4 Serial Transfer from Register A to register B

6.2 SHIFT REGISTERS - Serial Transfer

Serial-Transfer Example

Timing pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After T ₁	1 1 0 1	1 0 0 1	1
After T ₂	1 1 1 0	1 1 0 0	0
After T ₃	0 1 1 1	0 1 1 0	0
After T ₄	1 0 1 1	1 0 1 1	1

6.2 SHIFT REGISTERS - Serial Addition

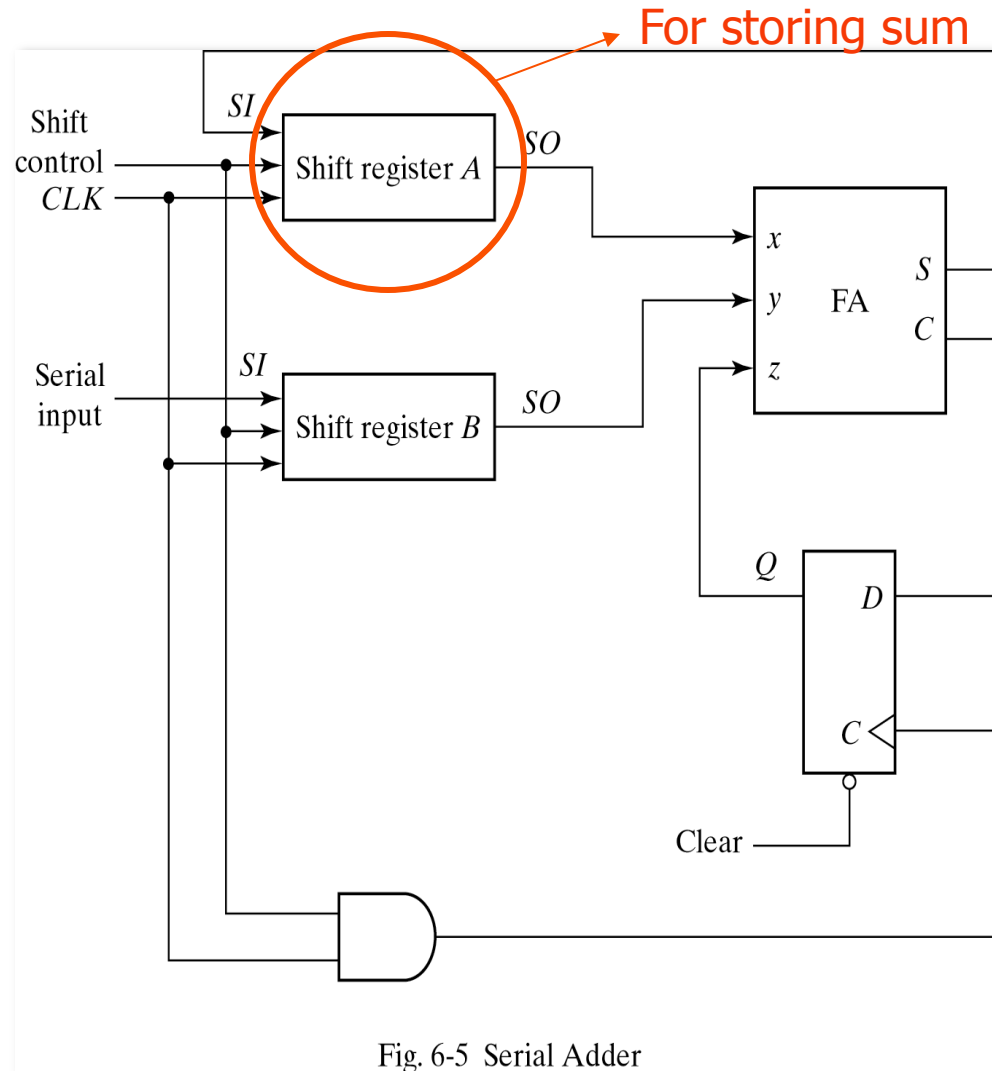

Operation

- the **A** register -
> augend, the **B** register -
> addend, carry $\rightarrow 0$
- The **SO** of **A** and **B** provide a pair of significant bits for the **FA**
- Output **Q** gives the input carry at **z**
- The shift-right control enables both registers and the carry flip-flop.
- The sum bit from **S** enters the leftmost flip-flop of **A**

6.2 SHIFT REGISTERS - State Table for Serial Adder

Table 6-2
State Table for Serial Adder

Present State	Inputs		Next State	Output	Flip-Flop Inputs	
	X	y			J_Q	K_Q
Q			Q	S		
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

Present value of carry

Output carry

$$J_Q = xy$$

$$K_Q = x'y' = (x + y)'$$

$$S = x \oplus y \oplus Q$$

By k-map

6.2 SHIFT REGISTERS - Second form of Serial Adder


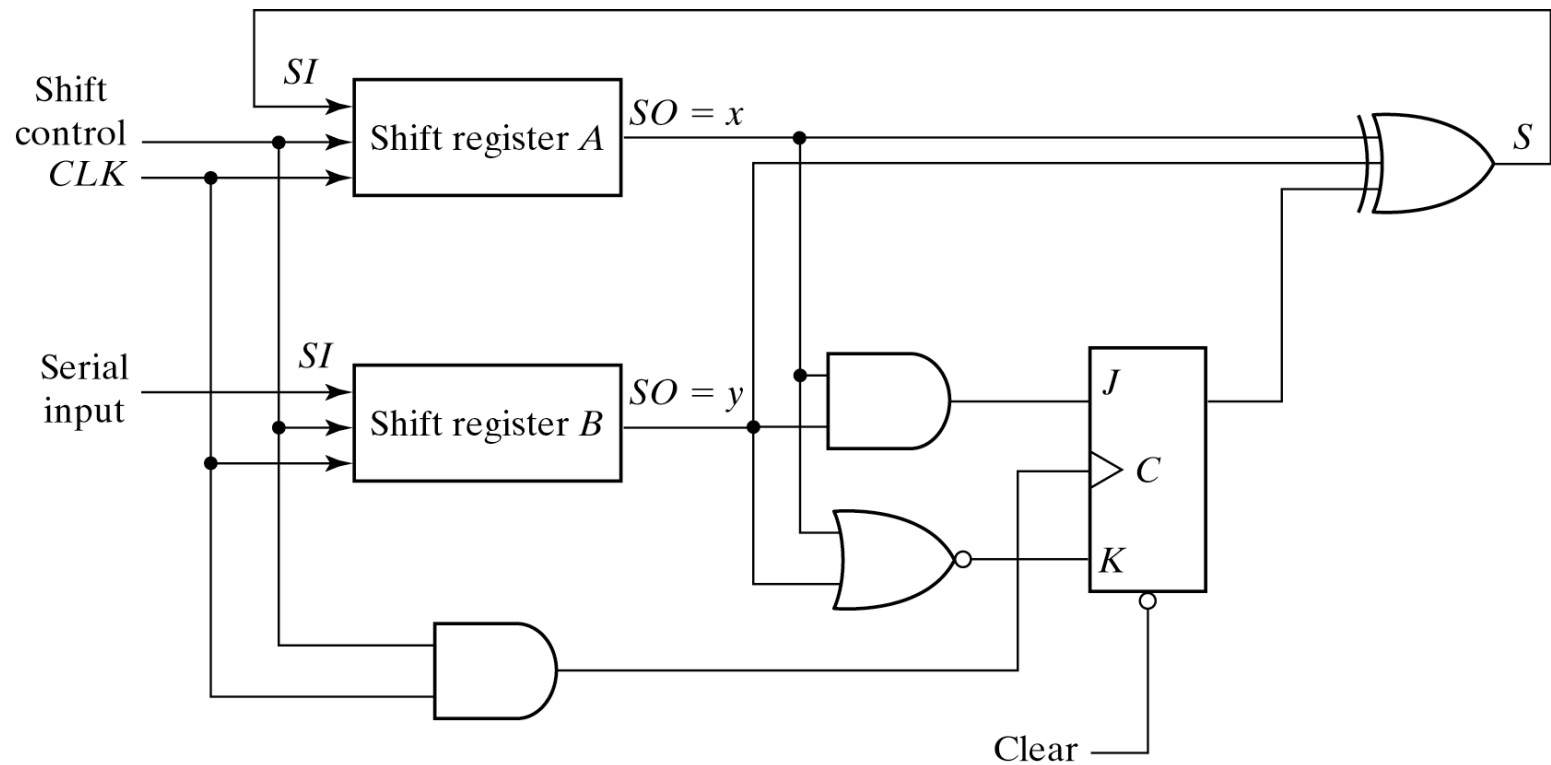


Fig. 6-6 Second form of Serial Adder

6.2 SHIFT REGISTERS - Second form of Serial Adder

● Universal Shift Register

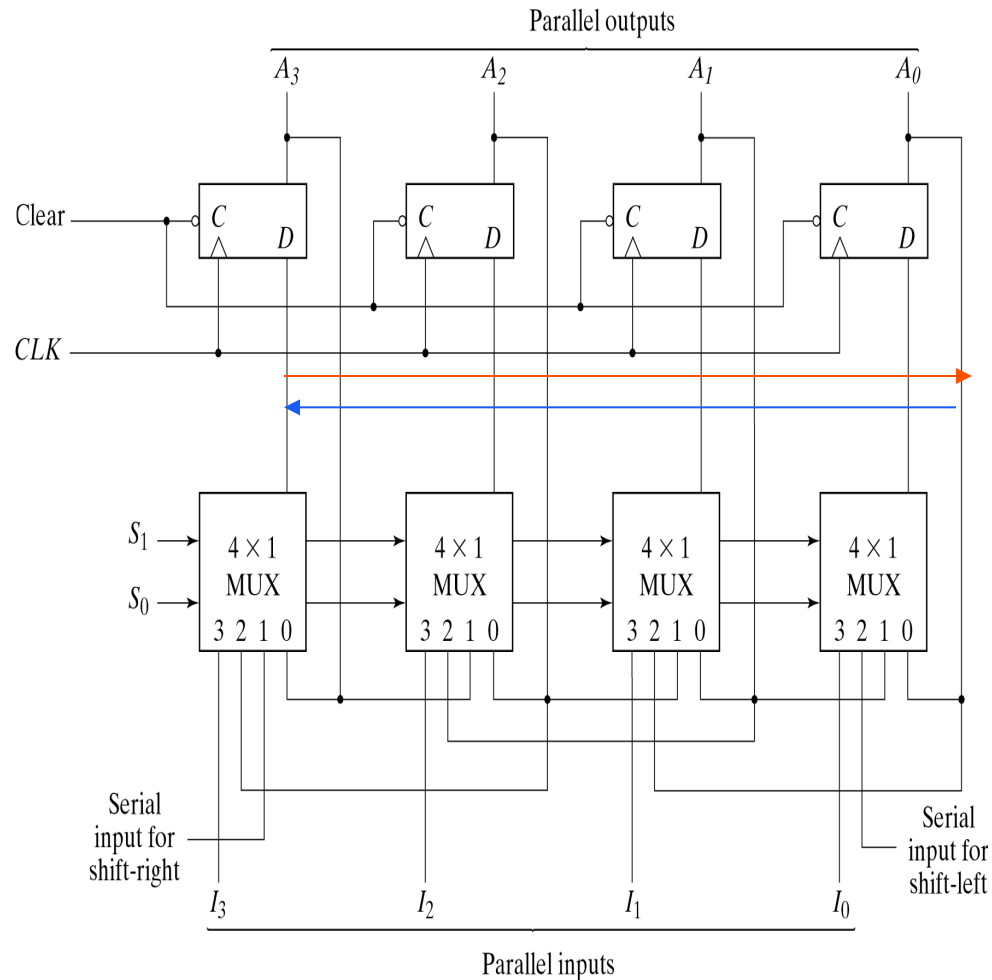

□ $S_1, S_0 \rightarrow 0, 0$; No change


□ $S_1, S_0 \rightarrow 0, 1$; Shift right

□ $S_1, S_0 \rightarrow 1, 0$; Shift left


□ $S_1, S_0 \rightarrow 1, 1$; Parallel load

Fig. 6-7 4-Bit Universal Shift Register

6.3 RIPPLE COUNTERS

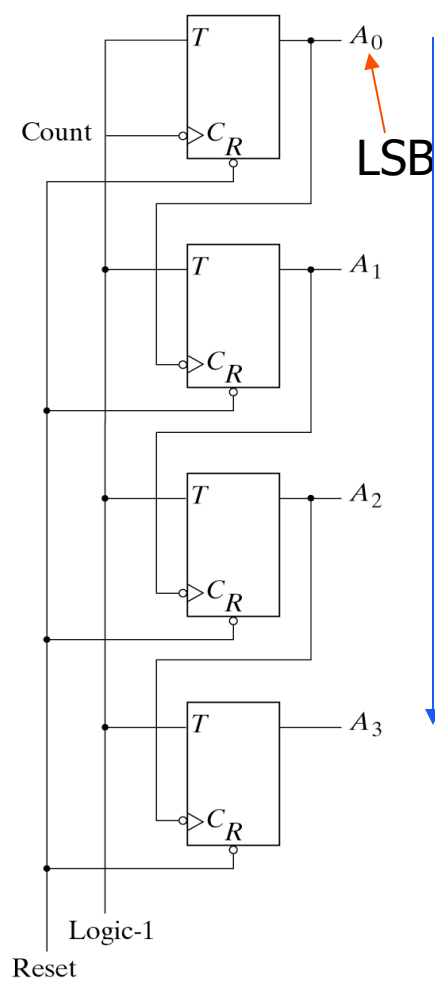

(a) With T flip-flops

 

(b) With D flip-flops

Fig. 6-8 4-Bit Binary Ripple Counter

6.3 RIPPLE COUNTERS - Binary Ripple Counter

Count sequence A₃ A₂ A₁ A₀		Conditions for Complementing
0 0 0 0	Complement A ₀	
0 0 0 1	Complement A ₀	A ₀ will go from 1 to 0 and complement A ₁
0 0 1 0	Complement A ₀	
0 0 1 1	Complement A ₀	A ₀ will go from 1 to 0 and complement A ₁ ;
0 1 0 0	Complement A ₀	A ₁ will go from 1 to 0 and complement A ₂
0 1 0 1	Complement A ₀	
0 1 1 0	Complement A ₀	A ₀ will go from 1 to 0 and complement A ₁
0 1 1 1	Complement A ₀	
.....		
1 0 0 0	and so on...	

6.3 RIPPLE COUNTERS - BCD Ripple Counter

 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

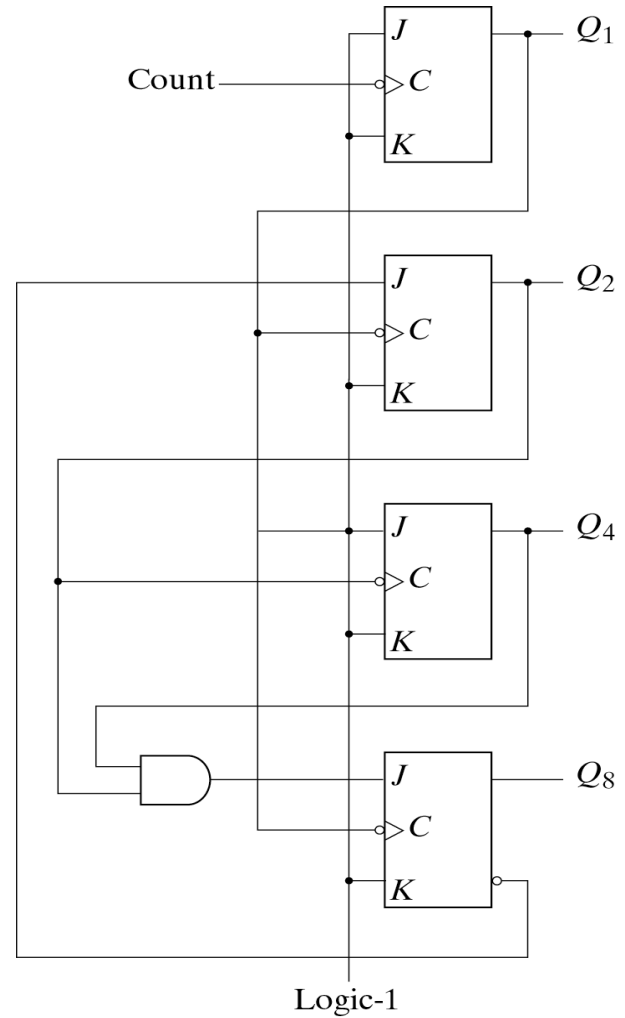


Fig. 6-10 BCD Ripple Counter

6.3 RIPPLE COUNTERS - BCD Ripple Counter

● Operation

1. Q_1 is complemented on the negative edge of every count pulse.
2. Q_2 is complemented if $Q_8=0$ and Q_1 goes from 1 to 0. Q_2 is cleared if $Q_8=1$ and Q_1 goes from 1 to 0.
3. Q_4 is complemented when Q_2 goes from 1 to 0.
4. Q_8 is complemented when $Q_4Q_2=11$ and Q_1 goes from 1 to 0. Q_8 is cleared if either Q_4 or Q_2 is 0 and Q_1 goes from 1 to 0.

6.3 RIPPLE COUNTERS - BCD Ripple Counter

● Three-Decade Decimal BCD Counter

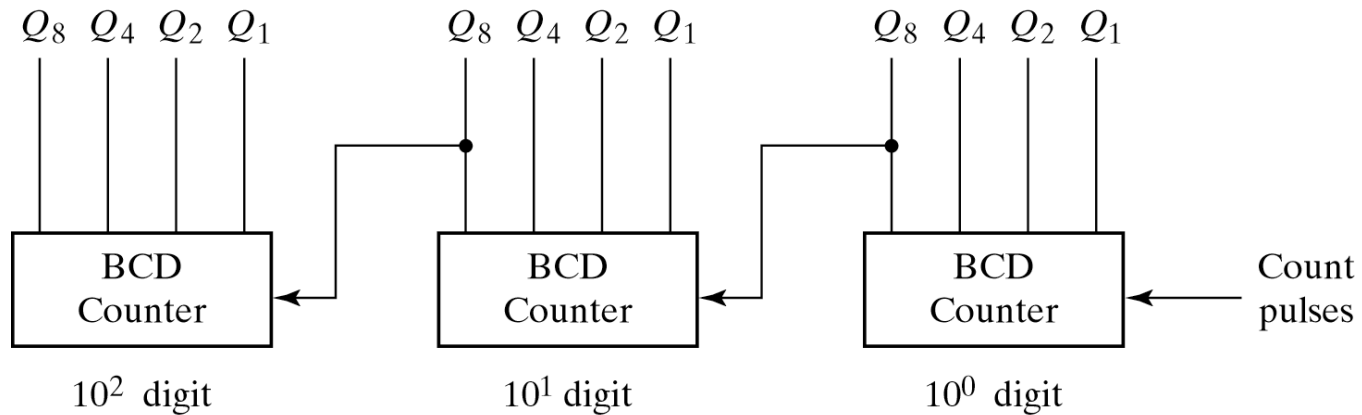



Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

❑ To count from **0** to **999**, We need a three-decade counter.

6.4 SYNCHRONOUS COUNTERS

- Synchronous Counters
 - Binary Counter
 - Up-Down Binary Counter
 - BCD Counter
 - Binary Counter with Parallel Load
 - Other Counter

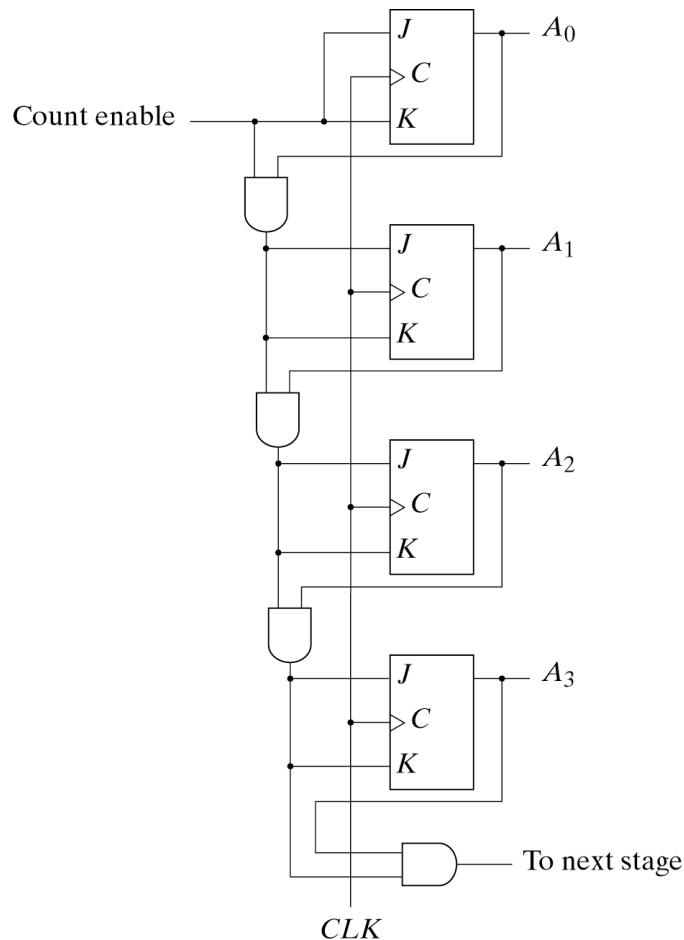6.4 SYNCHRONOUS COUNTERS - Binary Counter



❑ The first stage **A₀** has its **J** and **K** equal to **1** if the counter is enabled .

❑ The other **J** and **K** inputs are equal to **1** if all previous low-order bits are equal to **1** and the count is enabled.

Fig. 6-12 4-Bit Synchronous Binary Counter

6.4 SYNCHRONOUS COUNTERS - Up-Down Binary Counter

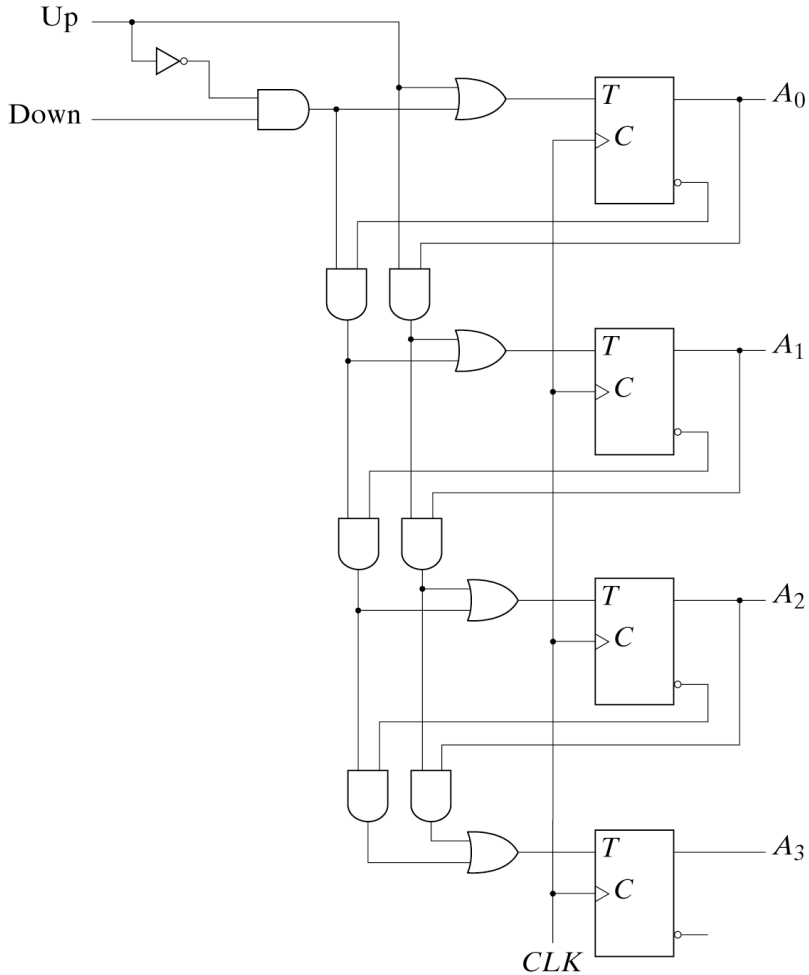


Fig. 6-13 4-Bit Up-Down Binary Counter

- ❑ **Up** input control=1 ;count up (the **T** inputs receive their signals from the values of the previous normal outputs of the flip-flops.)
- ❑ **Down** input control=1, **up** input control=0 ; count down
- ❑ **Up=down=0** ;unchanged state
- ❑ **Up=down=1** ;count up

6.4 SYNCHRONOUS COUNTERS - BCD Counter

Table 6-5
State Table for BCD Counter

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$$T_{Q1} = 1$$

$$T_{Q2} = Q'_8 Q_1$$

$$T_{Q4} = Q_2 Q_1$$

$$T_{Q8} = Q_8 Q_1 + Q_4 Q_2 Q_1$$

$$y = Q_8 Q_1$$

6.4 SYNCHRONOUS COUNTERS - Binary Counter with Parallel Load

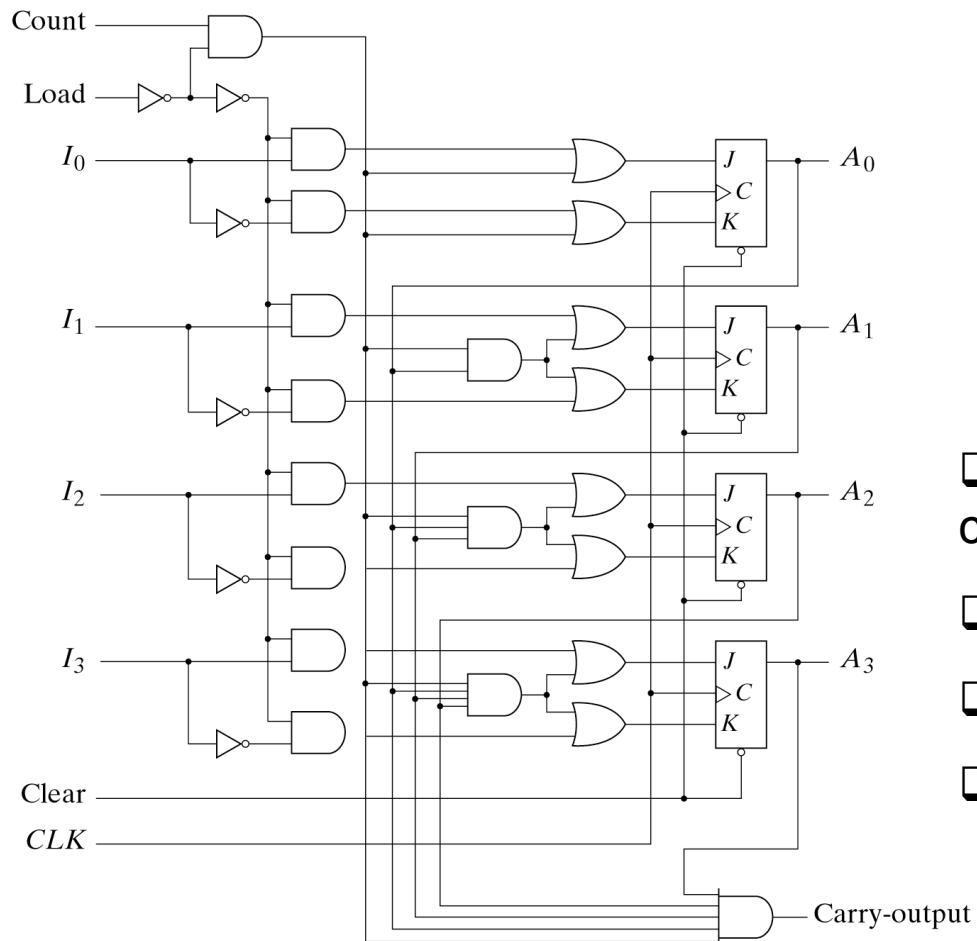


Fig. 6-14 4-Bit Binary Counter with Parallel Load

- ❑ Input **load** control=1 ; disables the count sequence ,data transfer
- ❑ **Load** =0 and **count**=1 ;count
- ❑ **Load**=0 and **count**=0 ;unchanged
- ❑ **Carry out**=1(all flip-flop=1)

6.4 SYNCHRONOUS COUNTERS - Binary Counter with Parallel Load

BCD COUNTER using Binary Counter with Parallel Load

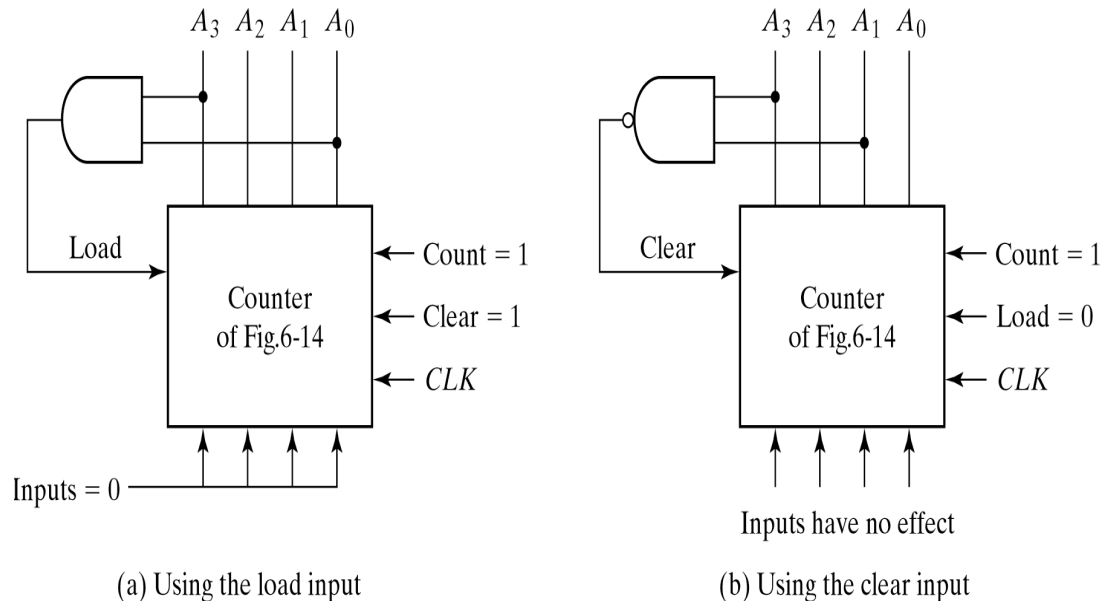


Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load

❑ The **AND** gate detects the occurrence of state **1001 (9)** in the output. In this state, the load input is enabled and all-**0**'s input is loaded into register.


❑ The **NAND** gate detects the count of **1010 (10)**, as soon as this count occurs the register is **cleared**.

❑ A momentary **spike** occurs in output A₂ as the count goes from **1001** to **1010** and immediately to **0000**.

6.5 OTHER COUNTERS

- Counter with Unused States
 - Don't care conditional Counter
- Ring Counter
- Johnson Counter

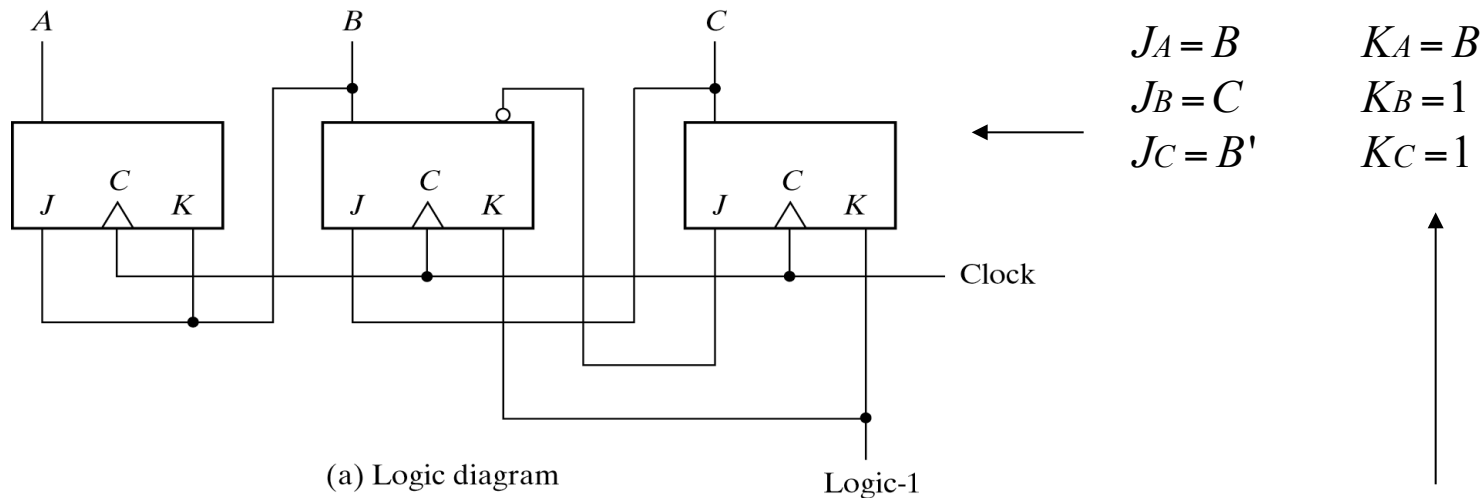6.5 OTHER COUNTERS - Counter with Unused States



Except **011, 111**

 


Fig. 6-16 Counter with Unused States

Table 6-7
State Table for Counter

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

6.5 OTHER COUNTERS - Ring Counter


 
 


Fig. 6-17 Generation of Timing Signals

❑ A circular shift register with only one flip-flop being set at any **particular time**. ; all others are cleared.

❑ **The single bit** is shifted from one flip-flop to the other.

6.5 OTHER COUNTERS - Johnson Counter

 

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

❑ A circular shift register with the complement output of the last flip-flop connected to the input of the first flip-flop.

Fig. 6-18 Construction of a Johnson Counter

7.1 INTRODUCTION

● Memory

RAM(random access memory): read and write operation

ROM(read only memory) : only read operation


● Programmable Logic Device

PLD(programmable logic device)


PLA(programmable logic array)

PAL(programmable array logic)

FPGA(field programmable gate array)

 


(a) Conventional symbol

 

(b) Array logic symbol

Fig. 7-1 Conventional and Array Logic Diagrams for OR Gate

7.2 RANDOM-ACCESS MEMORY

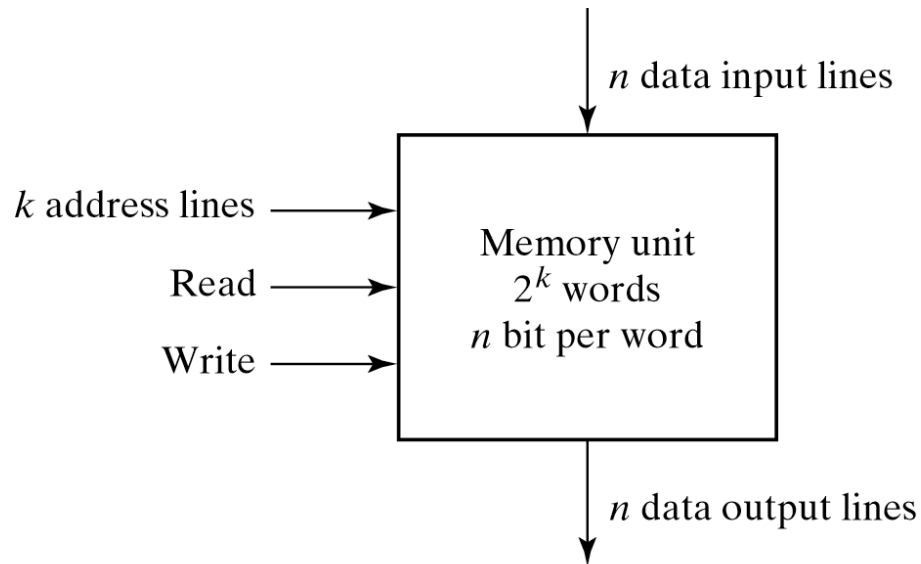

- ❑ The address lines select one particular word.
- ❑ A decoder inside the memory accepts this address and opens the paths needed to select the word specified.

Fig. 7-2 Block Diagram of a Memory Unit

7.2 RANDOM-ACCESS MEMORY

1024x16 Memory

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

The 1K * 16 memory has 10 bits in the address and 16 bits in each word.

7.2 RANDOM-ACCESS MEMORY - Write and Read Operations

☐ Write operation

1. Transfer the binary address of the desired word to the address lines.
2. Transfer the data bits that must be stored in memory to the data input lines.
3. Activate the write input

☐ Read operation

1. Transfer the binary address of the desired word to the address lines.
2. Activate the read input.

Table 7.1
Control Inputs to Memory Chip

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

7.2 RANDOM-ACCESS MEMORY - Timing Waveforms

 


Fig. 7-4 Memory Cycle Timing Waveforms

7.2 RANDOM-ACCESS MEMORY - Types of Memories

- ❑ **Random access Memory** -each word occupy one particular location.the access time is always the same
- ❑ **Sequential access Memory**-information is read out only when the required word has been reached. the access time is variable.
- ❑ **Volatile** -Memory units lose the stored information when power is turned off.
- ❑ **Nonvolatile**-A nonvolatile memory retains its stored information after removal of power. ex) magnetic disk ,ROM(Read Only Memory)
- ❑ **Static RAM**-The stored information remains valid as long as power is applied to the unit. Static **RAM** is easier to use and has shorter read and write cycles.
- ❑ **Dynamic RAM**-The capacitors must be periodically recharged by refreshing the dynamic memory. Dynamic **RAM** offers reduced power consumption and larger storage capacity

7.3 MEMORY DECODING - Internal Construction

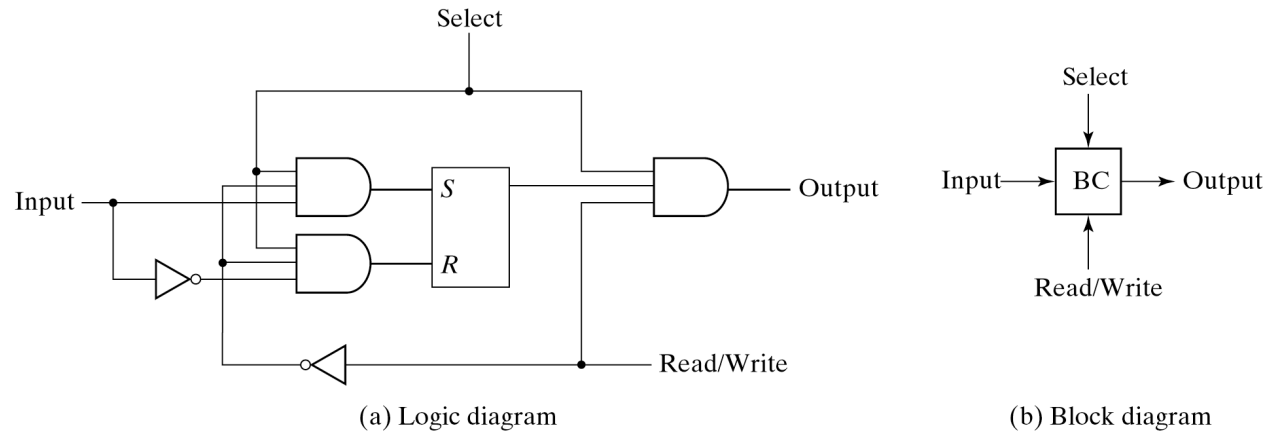


Fig. 7-5 Memory Cell

- ❑ The equivalent logic of a binary cell that stores one bit of information
- ❑ The binary cell stores one bit in its internal flip-flop
- ❑ It has three inputs and one output. The read/write input determines the cell operation when it is selected.

7.3 MEMORY DECODING - Internal Construction

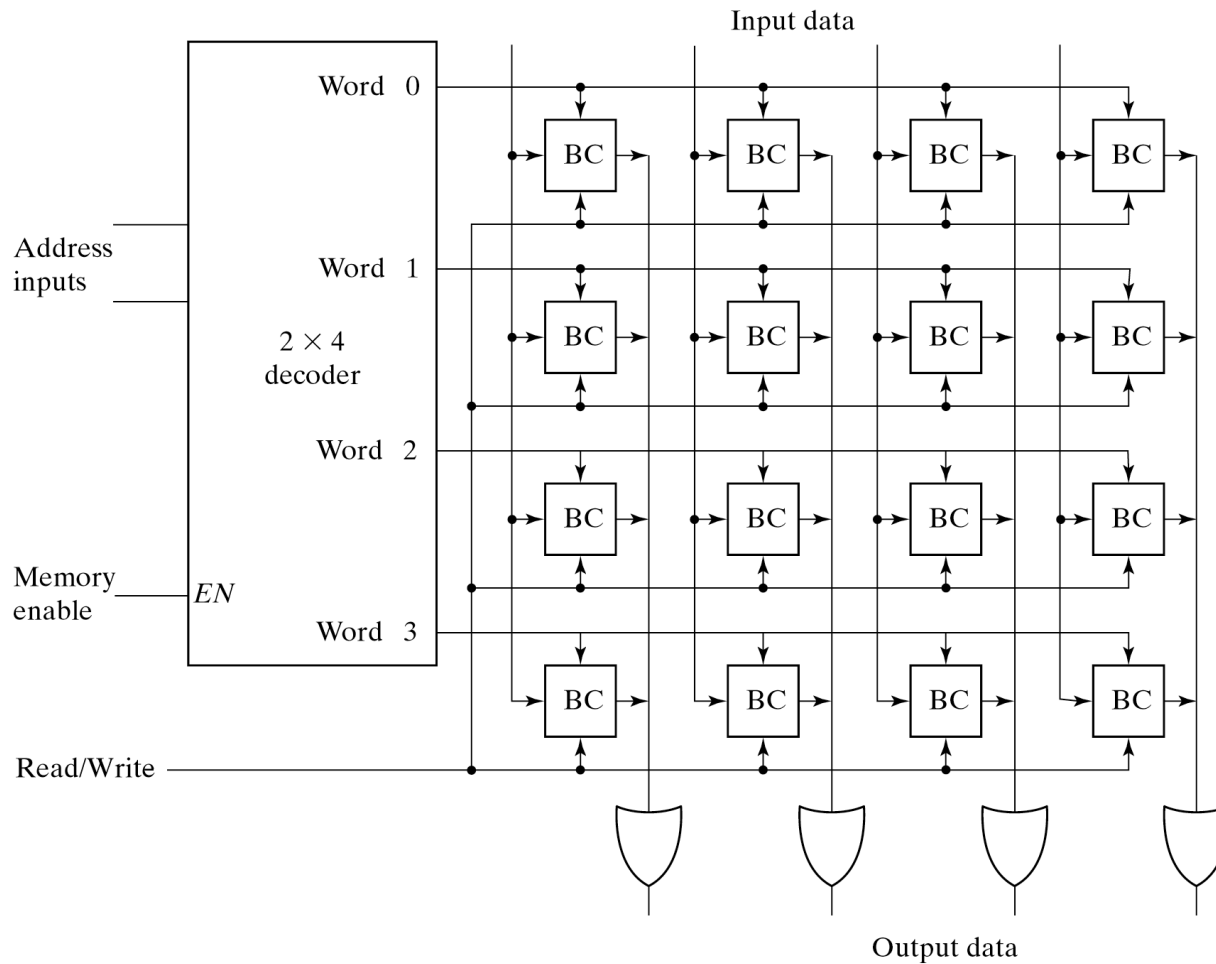


Fig. 7-6 Diagram of a 4×4 RAM

7.3 MEMORY DECODING - Internal Construction

- ❑ It has 16 binary cells
- ❑ Memory enable=0; all outputs of the decoder =0 , none of the memory words are selected.
- ❑ Memory enable=1; one of the four words is selected. The read/write input determines the operation.
- ❑ During the read operation, the four bits of the selected word go through **OR** gates to the output terminals.
- ❑ During the write operation, the data available in the input lines are transferred into the four binary cells of the selected word.

7.3 MEMORY DECODING - Coincident Decoding

 


Fig. 7-7 Two-Dimensional Decoding Structure for a 1K-Word Memory

❑ The basic idea in two-dimensional decoding is to arrange the memory cells in an array that is close as possible as square. In this configuration, two $k/2$ -input decoders are used instead of one k -input decoder.

❑ In the two-decoder case, we need 64 AND gates with five inputs in each.

❑ If the word address is 404, $X=01100$ (12) and $Y=10100$ (20).

7.3 MEMORY DECODING - Address Multiplexing

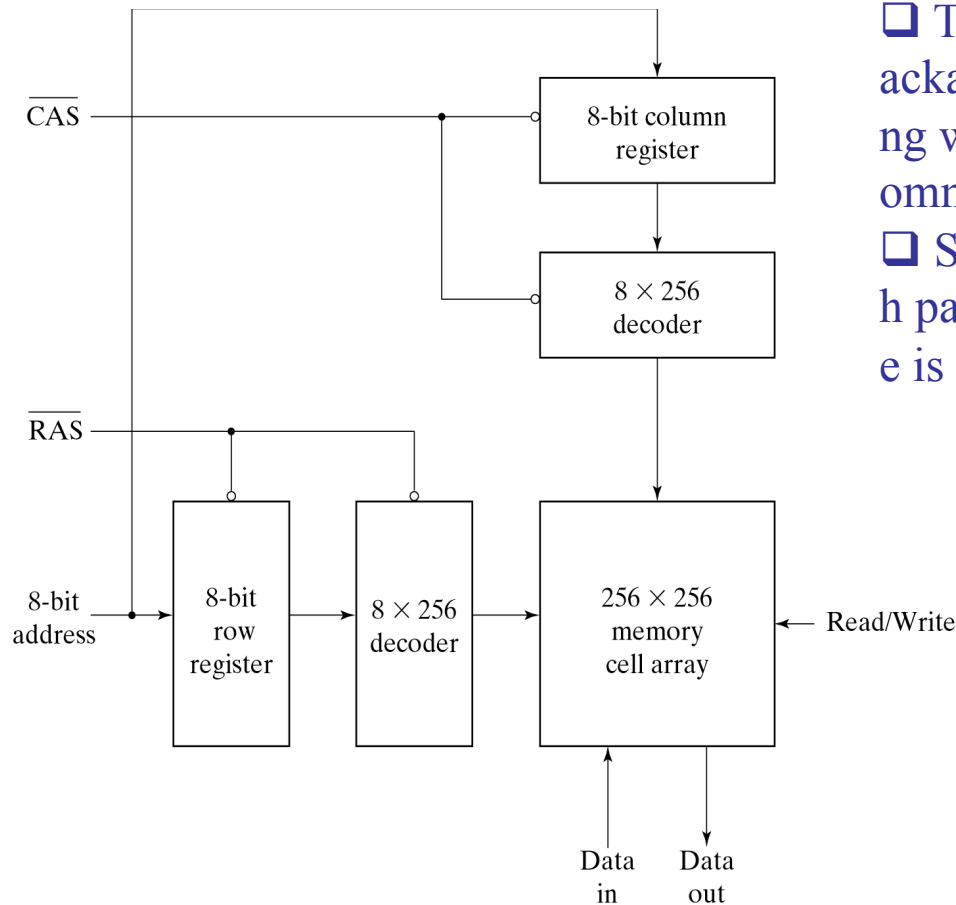


Fig. 7-8 Address Multiplexing for a 64K DRAM

- ❑ To reduce the number of pins in the IC package, designers utilize address multiplexing whereby one set of address input pins accommodates the address components.
- ❑ Since the same set of pins is used for both parts of the address, the size of the package is decreased significantly.

7.4 ERROR DETECTION AND CORRECTION

8-bit data word => 11000100

Bit position 1 2 3 4 5 6 7 8 9 10 11 12

P_1 P_2 1 P_4 1 0 0 P_8 0 1 0 0

P_1 =**XOR** of bits(3,5,7,9,11)=0 (**XOR** performs the odd function.)

P_2 =**XOR** of bits(3,6,7,10,11)=0

P_4 =**XOR** of bits(5,6,7,12)=1

P_8 =**XOR** of bits(9,10,11,12)=1

In memory, **Bit position** 1 2 3 4 5 6 7 8 9 10 11 12

0 0 1 1 1 0 0 1 0 1 0 0

When the 12 bits are read from memory ,The four check bits

C_1 =**XOR** of bits (1,3,5,7,9,11) C_2 =**XOR** of bits (2,3,6,7,10,11)

C_3 =**XOR** of bits (4,5,6,7,12) C_4 =**XOR** of bits (8,9,10,11,12)

7.4 ERROR DETECTION AND CORRECTION - Hamming code

Since the bits were stored with even parity $C=C_8C_4C_2C_1=0000$ (No error)

Bit position 1 2 3 4 5 6 7 8 9 10 11 12

0 0 1 1 1 0 0 1 0 1 0 0 **No error**

1 0 1 1 1 0 0 1 0 1 0 0 **Error in bit 1**

0 0 1 1 0 0 0 1 0 1 0 0 **Error in bit 5**

Check bits C_8 C_4 C_2 C_1

With error in bit 1 : 0 0 0 0

With error in bit 5: 0 1 0 1

The error can be corrected by complementing the corresponding bit.

7.4 ERROR DETECTION AND CORRECTION

- Single-Error Correction , Double-Error Detection

The **Hamming code** can detect and correct only a single error. Multiple errors are not detected.

To correct a single error and detect double errors ,we **include the additional parity bit**.

If $C=0$ and $P=0$ No error occurred

If $C=1$ and $p=1$ A single error occurred , which can be corrected

If $C=1$ and $P=0$ A double error occurred, which is detected but cannot be corrected

If $C=0$ and $P=1$ An error occurred in the P_{13} bit

7.5 READ-ONLY MEMORY

ROM=Decoder + OR gates

-permanent binary information is stored.

 


Fig. 7-9 ROM Block Diagram

k input lines and n output lines

The number of output lines , n = the number of bits per word

7.5 READ-ONLY MEMORY

ROM = **AND** gates connected as a decoder + a number of **OR** gates
5 X 32 decoder has 32 **AND** gates and 5 inverters.

 


Fig. 7-10 Internal Logic of a 32 x 8 ROM


7.5 READ-ONLY MEMORY

● ROM Truth Table(Partial)

Table 7-3
ROM Truth Table (Partial)

Inputs					Outputs							
I4	I3	I2	I1	I0	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮					⋮					
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

 7.5 READ-ONLY MEMORY - Combinational Circuit Implementation



$A_7(I_4, I_3, I_2, I_0) = \text{Sum of minterms}(0, 2, 3, \dots, 29)$

Input $\rightarrow 00011(3)$

Others \rightarrow all '0'

Output $\rightarrow 10110010$

Fig. 7-11 Programming the ROM According to Table 7-3

7.5 READ-ONLY MEMORY - Combinational Circuit Implementation

EXAMPLE 7-1

Table 7-4
Truth Table for Circuit of Example 7-1

Inputs			Outputs							Decimal
A_1	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0		
0	0	0	0	0	0	0	0	0	0	
0	0	1	0	0	0	0	0	1	1	
0	1	0	0	0	0	1	0	0	4	
0	1	1	0	0	1	0	0	1	9	
1	0	0	0	1	0	0	0	0	16	
1	0	1	0	1	1	0	0	1	25	
1	1	0	1	0	0	1	0	0	36	
1	1	1	1	1	0	0	0	1	49	

 


Fig. 7-12 ROM Implementation of Example 7-1

7.5 READ-ONLY MEMORY - Types of ROMs

For large quantities, **mask programming** is economical .

For small quantities , programmable read-only memory(**PROM**) is more economical.(all '1's)

PROM- irreversible and permanent

EPROM(Erasable PROM)- can be restructured to the initial value(UV light->discharge)

EEPROM(Electrically erasable PROM)- can be erased with electrical signals instead ultra violet light.

7.5 READ-ONLY MEMORY - Combinational PLDs

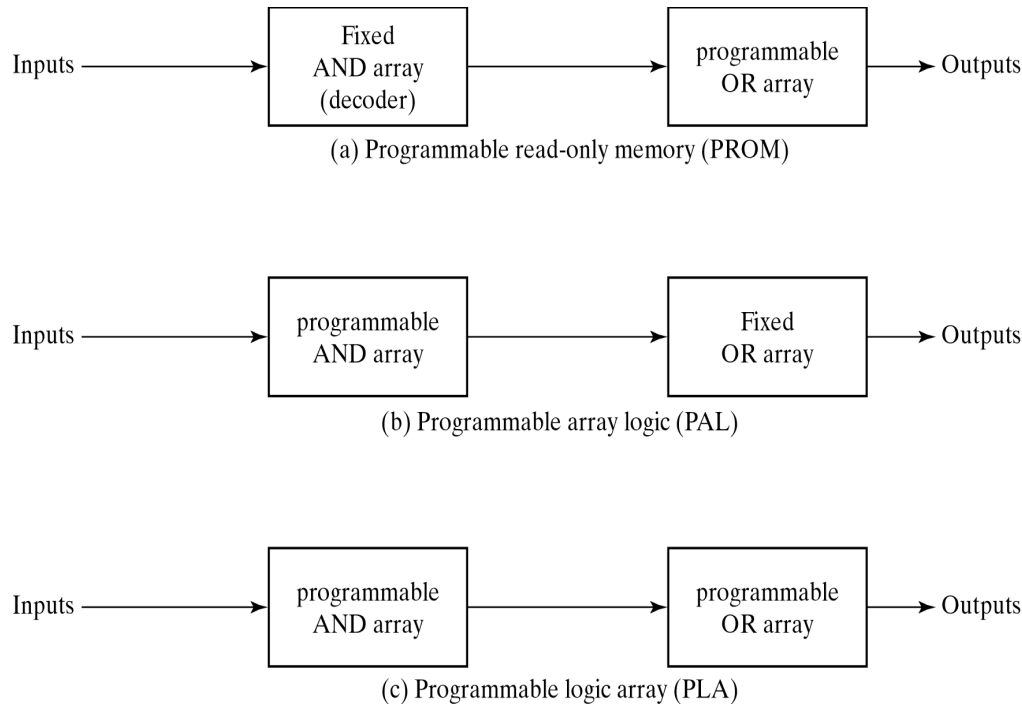


Fig. 7-13 Basic Configuration of Three PLDs

□ A combinational PLD is an IC with programmable gates divided into an **AND** array and an **OR** array to provide an **AND-OR** sum of product implementation.

□ Three major types PLDs

(a) fixed **AND** array + programmable **OR** array

(b) programmable **AND** array + fixed **OR** array

(c) programmable **AND** array + programmable **OR** array