


## Ch 5. Synchronous sequential logic

## 5.1 Introduction

- In order to perform useful or flexible sequences of operations, we need to be able to construct circuits that can store information between the operations.
- latches and Flip-Flops
- Sequential circuits consisting of both flip-flop and combinational logic

 
## 5.2 Sequential circuits

- Outputs are function of inputs and present states
- Present states are supplied by memory elements


 
## 5.2 Sequential circuits

- Two types of sequential circuit
- Synchronous : behavior depends on the signals affecting storage elements at discrete time
- Asynchronous : behavior depends on inputs at any instance of time



(a) Block diagram



(b) Timing diagram of clock pulses

## 5.3 Latches

- SR latch : consist of two cross-coupled NOR gates
- $S=1, R=0$  then  $Q=1$  (set)
- $S=0, R=1$  then  $Q=0$  (reset)
- $S=0, R=0$  then no change (keep condition)
- $S=1, R=1$   $Q=Q'=0$  (undefined)

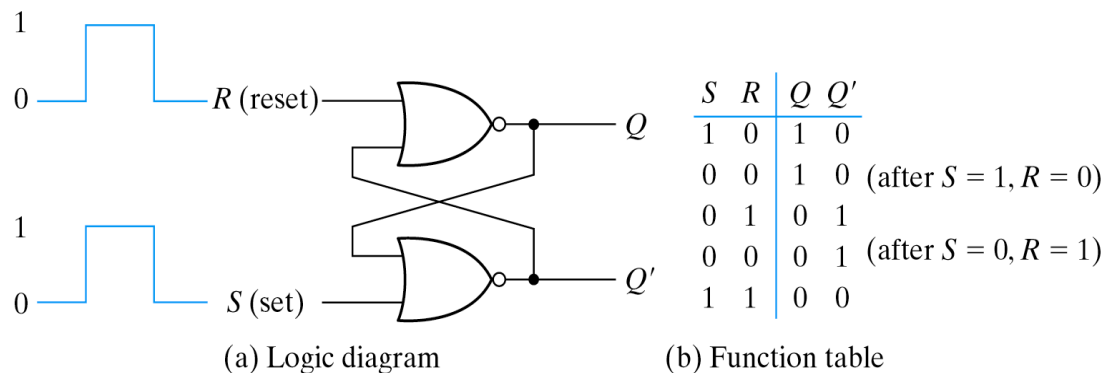


Fig. 5-3 SR Latch with NOR Gates

## 5.3 Latches - SR latch

- S'R' latch with NAND gates
  - Require the complement value of NOR latch


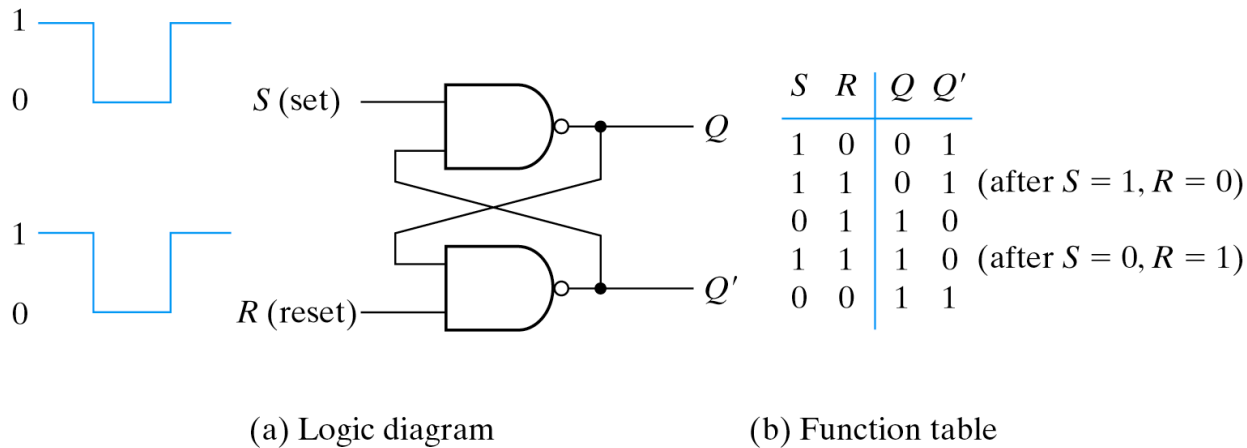


Fig. 5-4 SR Latch with NAND Gates
 
## 5.3 Latches - SR latch


- SR latch with control input
  - Add two NAND gate and control signal
  - $C=0$ (no action),  $C=1$ (act as SR latch)



(a) Logic diagram


$C$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table

 
 
## 5.3 Latches - D latch

- Eliminate indeterminate state in SR latch
  - $C=1$ , output value is equal to  $D$




(a) Logic diagram

$C$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; Reset state
1	1	$Q = 1$ ; Set state

(b) Function table


Fig. 5-6 D Latch

 


 
## 5.4 Flip-Flops

- Latch : case (a), output changes as input changes
- Flip-flop : output only changes at clock edge



## 5.4 Flip-flops - Edge-Triggered Flip-Flop

- Negative edge triggered D flip-flop
- $C=0$  : master disable, slave enable
- Output has no relation with input
- $C=1$  : master enable, slave disable


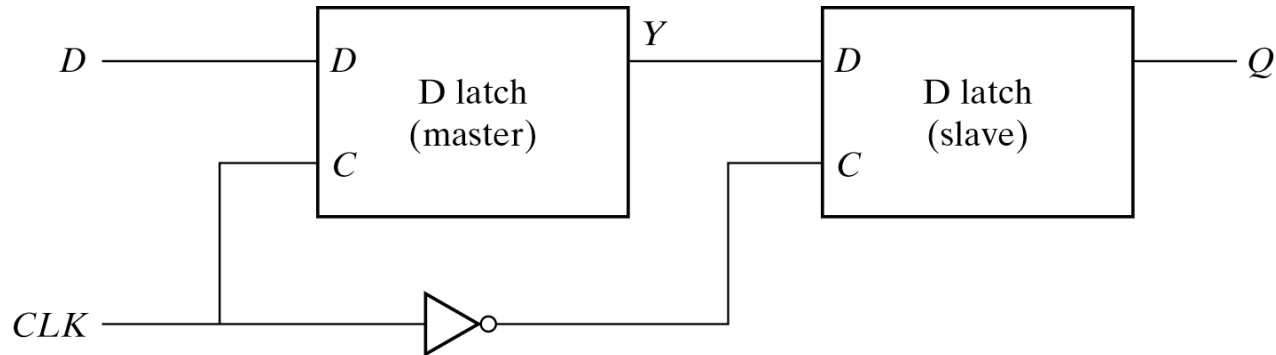


Fig. 5-9 Master-Slave  $D$  Flip-Flop

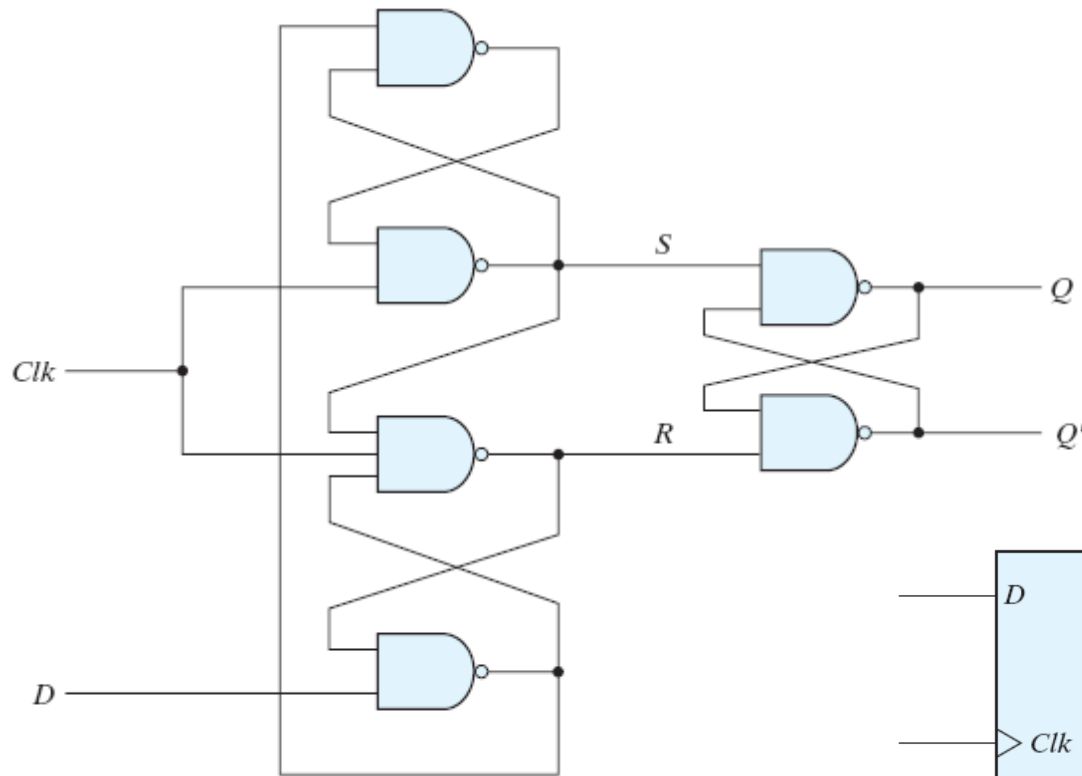
## 5.4 Flip-flops - Other Flip-Flop

- D-type positive edge triggered flip flop
  - Consist of 3 SR-latches
  - Q changes only when C becomes 0 to 1




**D Flip-Flop**

<i>D</i>	$Q(t + 1)$	
0	0	Reset
1	1	Set

 

(a) Positive-edge

 


(a) Negative-edge

## 5.4 Flip-flops - Other Flip-Flop


### ● JK flip-flop

- Performs three operations
- Set(J), Reset(K), Complement(J=K=1)
- $D = JQ' + K'Q$

<b>JK Flip-Flop</b>			
<i>J</i>	<i>K</i>	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

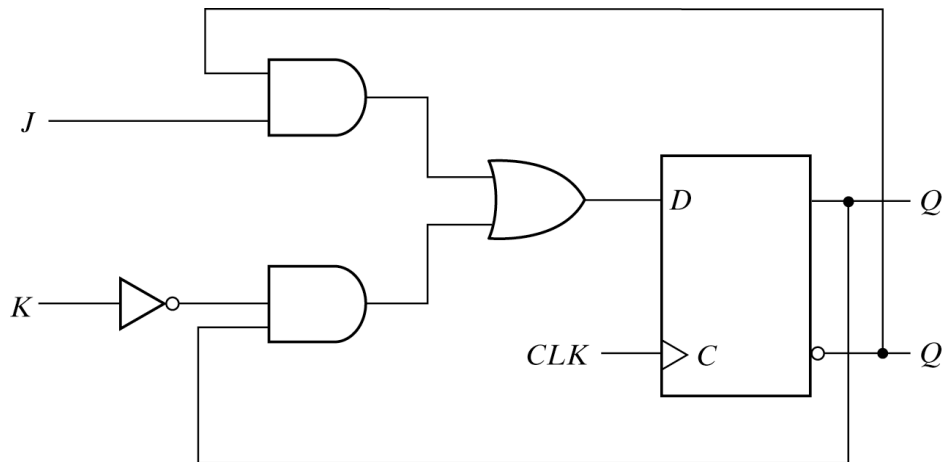

(a) Circuit diagram

 

(b) Graphic symbol

Fig. 5-12 JK Flip-Flop


## 5.4 Flip-flops - Other Flip-Flop

### ● T flip-flop


- Complementing flip-flop
- $D = TQ' + T'Q$

**T Flip-Flop**


$T$	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

 

(a) From JK flip-flop

 



(b) From D flip-flop

 

(c) Graphic symbol

Fig. 5-13 T Flip-Flop
 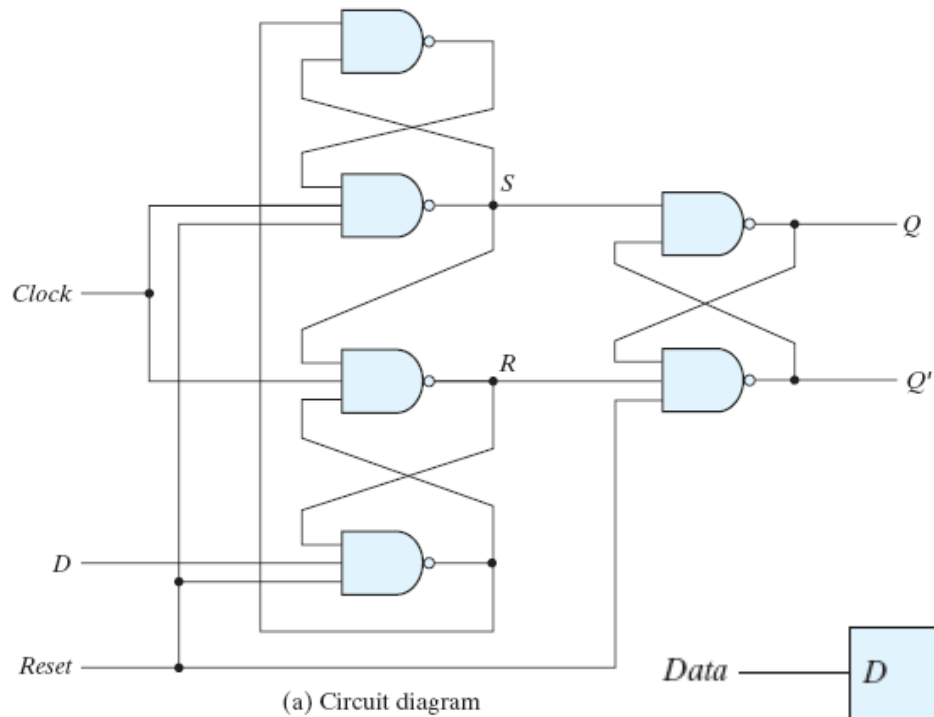
## 5.4 Flip-flops - Characteristic Equations




$R$	$Clk$	$D$	$Q$	$Q'$
0	X	X	0	1
1	$\uparrow$	0	0	1
1	$\uparrow$	1	1	0

(b) Function table
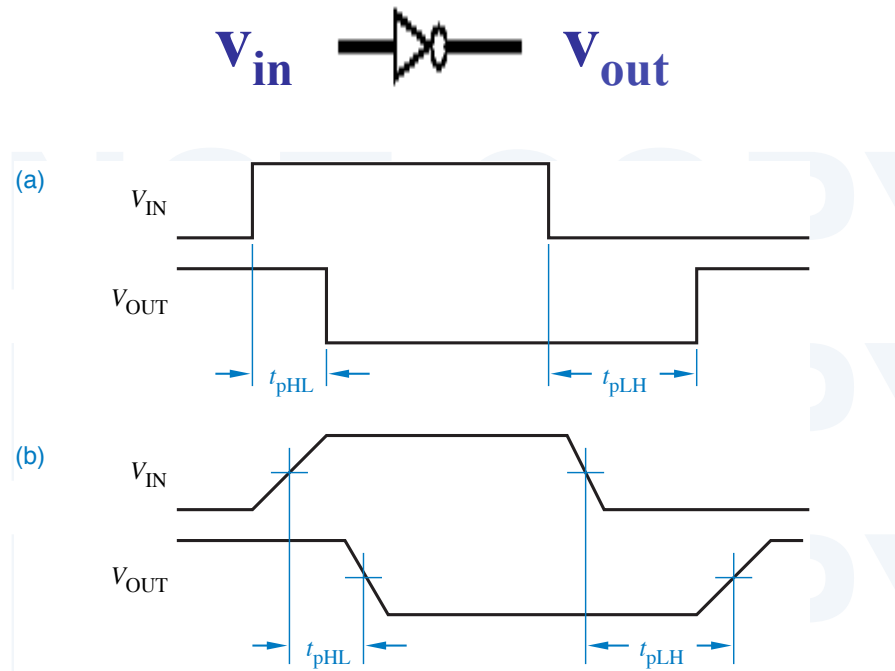
## 5.9 Timing

- Propagation Delay (Gate Delays)
  - Actual circuits need time to raise/bring down voltages
  - PD of a gate: output delay in response to input



## 5.9 Timing



- Gate delays
  - Delays adds up!
  - If a signal has to go through  $n$  gates
  - total delay

$$\sum_{i=1}^n t_i, \quad t_i \text{ is the gate delay of } i\text{th gate}$$

**FIGURE 8-5**

Timing Diagram for  
AND-NOR Circuit


© Cengage Learning 2014

  



 
## 5.9 Timing

- metastability
- Consider the following logic with feedback



 - There are three state possible:  $Q=0$ ,  $Q=1$  and  $Q \sim 0.5$ !




Transfer function:

$$V_{out1} = T(V_{in1})$$


$$V_{out2} = T(V_{in2})$$
 
## 5.9 Timing

- metastability
- Consider the following logic with feedback



 - If  $Q \sim 0.5$  we say the system is **metastable**



## 5.9 Timing: D-Latch


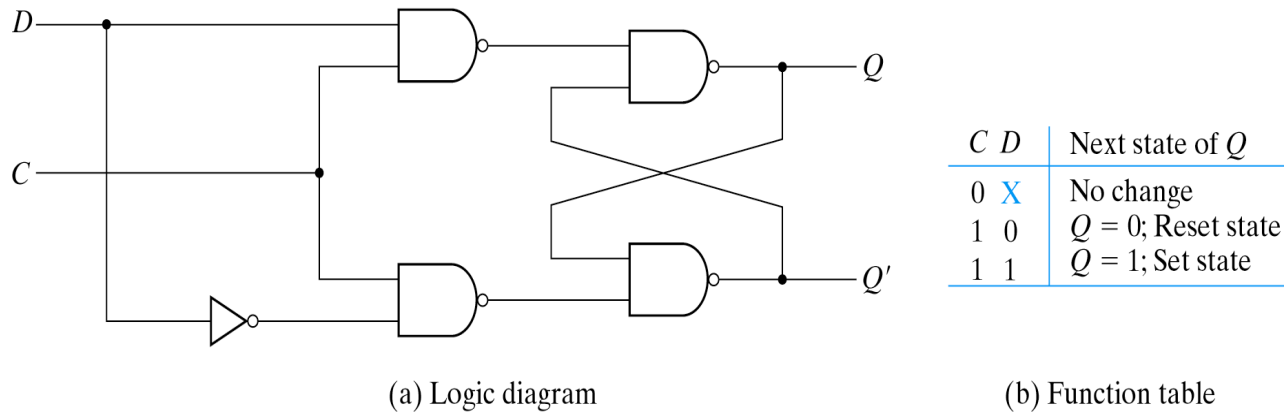


Fig. 5-6 D Latch


Figure 7-14 Timing parameters for a D latch.

 

● D should NOT change quickly when C also changes!
 
## 5.9 Timing

- Timing of positive-edge triggered flip-flop



- Setup time


- D should not change during  $t_{su}$  before clock edge

- Hold time

- D should not change during  $t_h$  after clock edge


**FIGURE 11-20**  
Setup and Hold  
Times for an  
Edge-Triggered D  
Flip-Flop

© Cengage Learning 2014

 


## 5.9 Timing

### Timing of positive-edge triggered D flip-flop

 


**Figure 7-17** Timing behavior of a positive-edge-triggered D flip-flop.

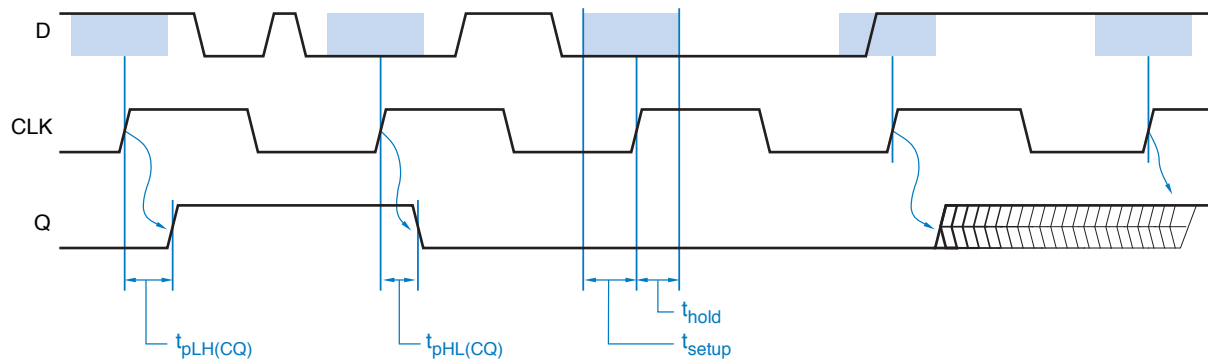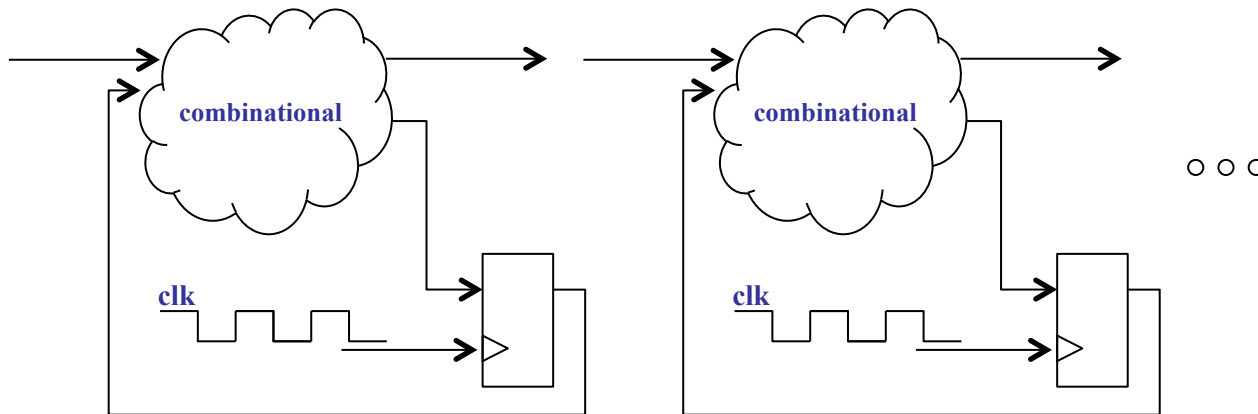


## 5.9 Timing

- Design of Sequential logic
  - Propagation (gate) delay should be considered to satisfy setup and hold time!



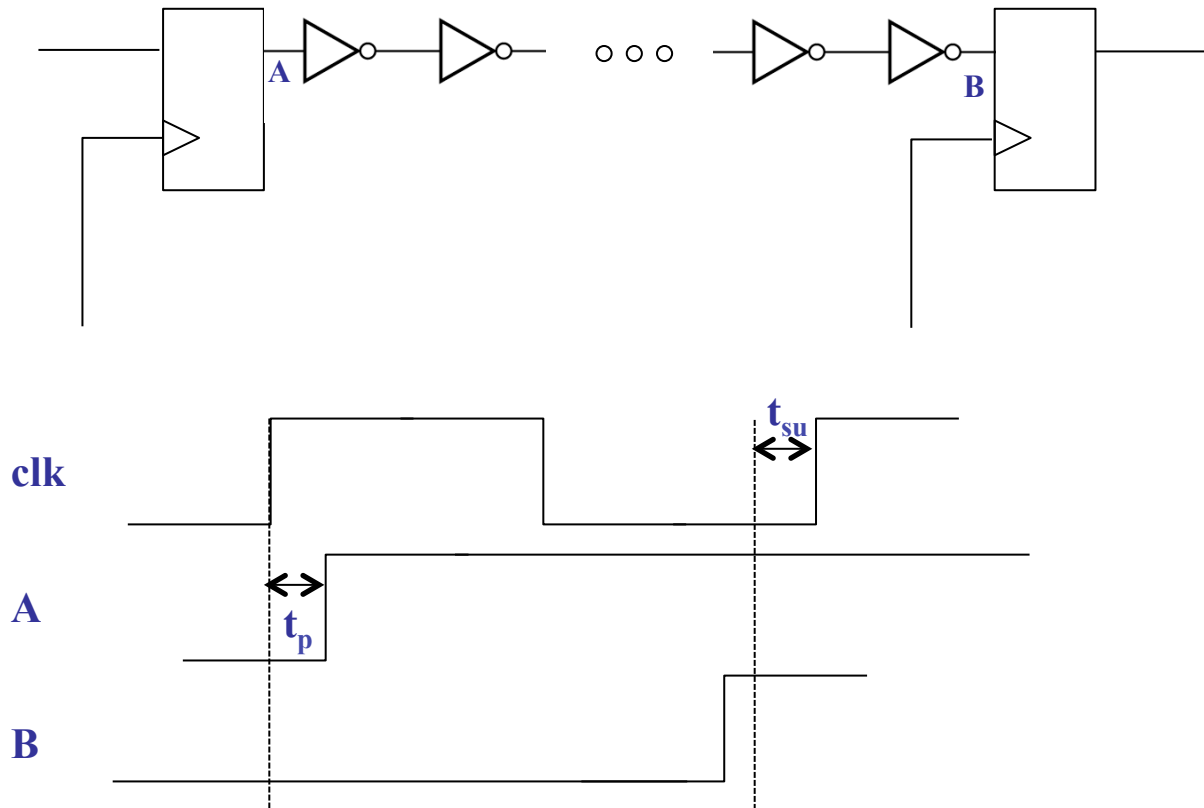
## 5.9 Timing

- Design of Sequential logic
  - Propagation (gate) delay should be considered to satisfy setup and hold time!


 
## 5.9 Timing


- Design of Sequential logic
  - Propagation (gate) delay should be considered to satisfy setup and hold time!





 
## 5.9 Timing

- Gate delays
  - What is the minimum # of gates a signal has to pass?
    - 2
  - What is the maximum # of gates a signal has to pass?
    - 3



 
## 5.9 Timing

- Critical path
  - a signal path with maximum total propagation delay
- Delay of combinational logic
  - determined by the critical path


 
## 5.9 Timing


- Clock period
  - length of one clock cycle
- Clock frequency
  - $1/t_{\text{clk}}$
  - unit: Hz (Hertz)



- Ex: consider a processor with frequency  $1\text{GHz} = 10^9 \text{ Hz}$ 
  - What is its period?
  - $1/10^9 = 10^{-9} \text{ sec} = 1 \text{ ns}$
- Most digital systems: runs by clock
- Clock frequency determines how fast your system is
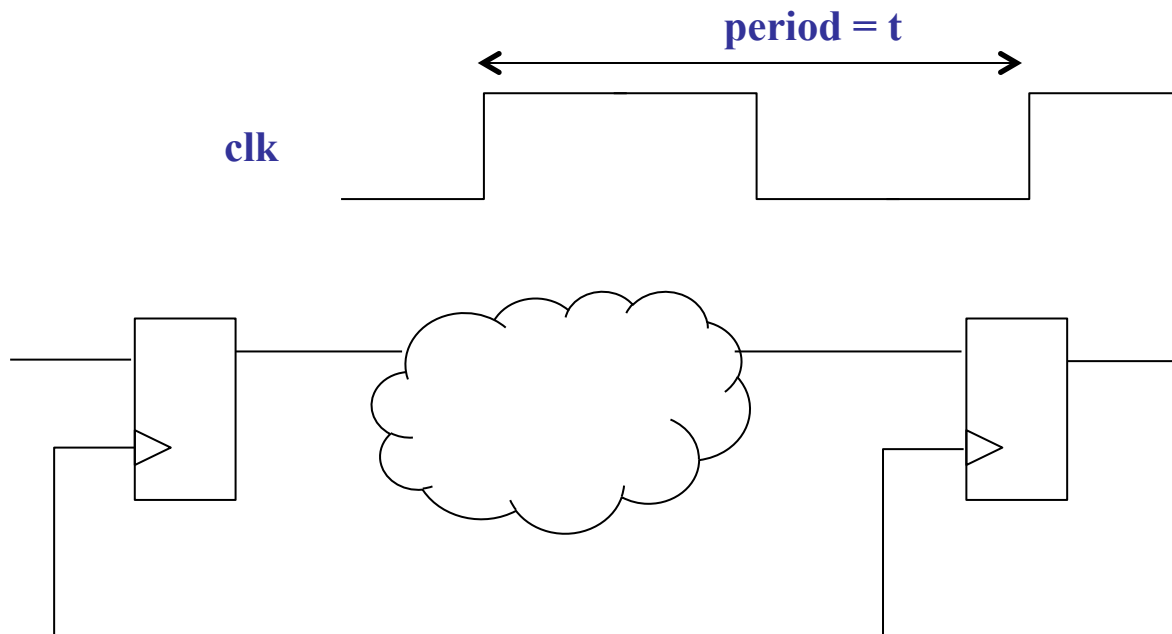
## 5.9 Timing

- Digital system with sequential logic
- All the critical paths must meet the timing of clock
- Clock period usually permits a critical path of 20~50 gates



## 5.9 Timing

- Lets say we allow 35 gates at maximum
- suppose clock frequency = 500 MHz  
clock period =  $(5 \times 10^8 \text{ s}^{-1})^{-1} = 2 \times 10^{-9} \text{ s} = 2 \text{ ns}$  (nanoseconds)
- Gate delay must be less than  
 $(1/35) \times \text{Period} = (2 \text{ ns})/35 = 57 \text{ ps}$  (picoseconds)
- How fast is this? Speed of light:  $c = 3 \times 10^8 \text{ m/s}$   
Distance traveled in 57 ps is:

$$(3 \times 10^8 \text{ m/s})(57 \times 10^{-12} \text{ s}) = 17 \times 10^{-4} \text{ m} = 1.7 \text{ cm}$$

## 5.5 Analysis of clocked sequential circuits

- Behavior of clocked sequential circuit is determined from input, output and present state
- Output, next state are a function of input and present state

## 5.5 Analysis of clocked sequential circuits

- Finite State Machine (FSM)
  - An abstract model of the operation of a (automated) system which is in one of the **states** at any given time. The state information is stored in the system
  - System may make transition to another state depending on the input and current state
  - System may produce an output
  - Many machinery can be modeled using FSM


## 5.5 Analysis of clocked sequential circuits

- Elements of FSM
- States
  - A specific status of the system at a given time
- Input
  - External information which determines the operation of the system
- Output
  - Generated by the system, may depend on state and input
- Transition
  - The system moves to another state



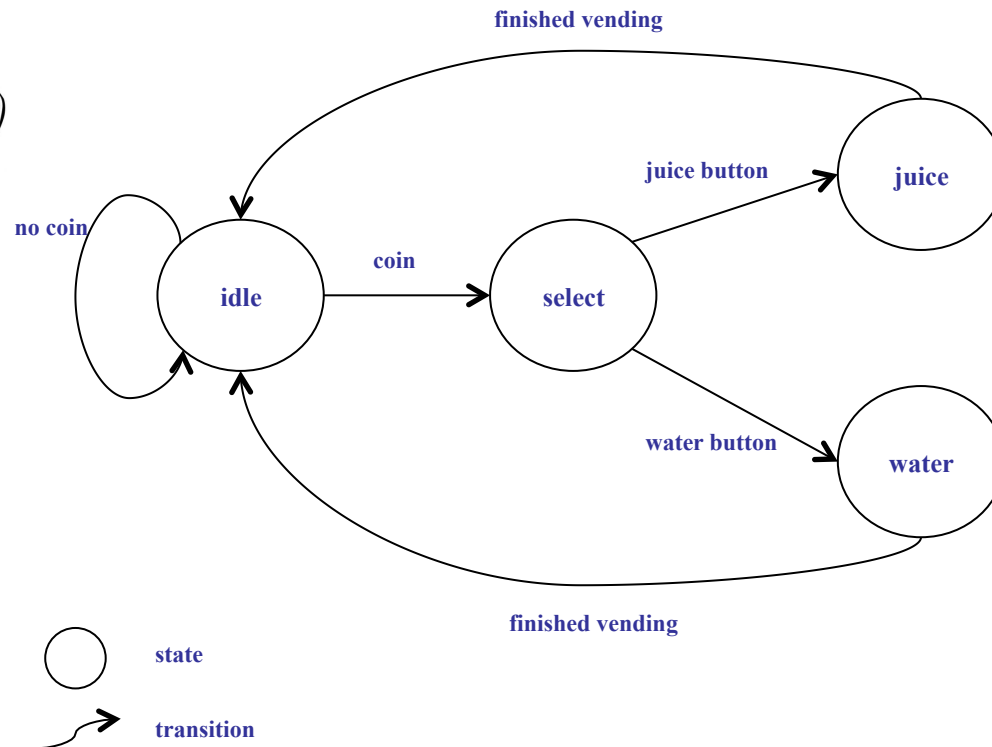- **Example: vending machine**

- **Operation of many systems (machines) can be described using FSM**




## 5.5 Analysis of clocked sequential circuits

- Synchronous FSM
  - System can make transition only at particular instants in time
  - In our case, we consider *clocked FSM*, which is a FSM synchronized at clock edges
    - That is, FSM can make transition at clock edges
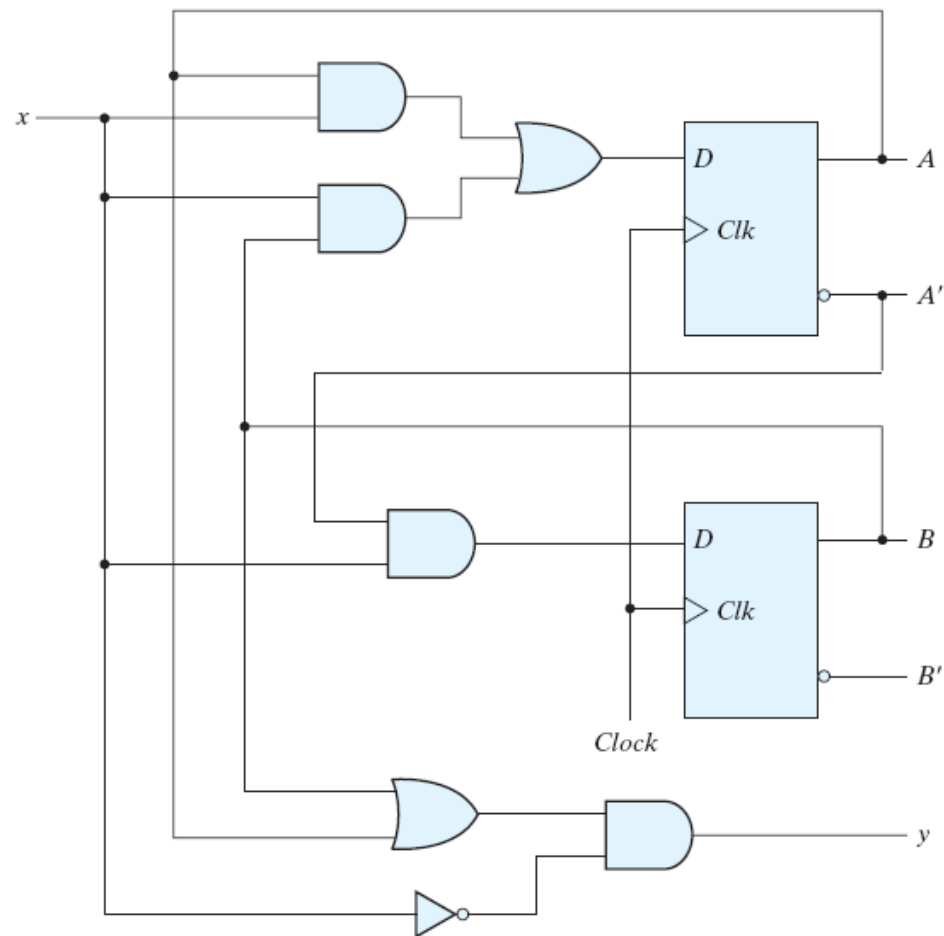
## 5.5 Analysis of clocked sequential circuits - State equations

- Specifies the next state and output as a function of the present state and inputs
- $A(t+1) = Ax + Bx$
- $B(t+1) = A'x$
- $Y = (A+B)x'$



## 5.5 Analysis of clocked sequential circuits - State table

- Time sequence table of inputs, outputs and flip-flop state
- two types of state table exist

**Table 5-2**  
*State Table for the Circuit of Fig. 5-15*

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

**Table 5-3**  
*Second Form of the State Table*

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
AB	AB	AB	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

## 5.5 Analysis of clocked sequential circuits - State diagram

- A kind of flow diagram
- Can be derived from state table
- State-circle, transition-line, I/O

**Table 5-2**

*State Table for the Circuit of Fig. 5-15*

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


 



Fig. 5-16 State Diagram of the Circuit of Fig. 5-15
 
## 5.5 Analysis of clocked sequential circuits - Analysis with D flip-flops

- Input equation :  $D_A = A \oplus x \oplus y$
- State equation is equal to input equation



(a) Circuit diagram

 

(c) State diagram

Present state	Inputs		Next state
$A$	$x$	$y$	$A$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

Fig. 5-17 Sequential Circuit with D Flip-Flop


## 5.5 Analysis of clocked sequential circuits - Analysis with JK flip-flops

- State equation is not the same as the input equation
- Have to refer characteristic table or characteristic equation

- Input equations

$$J_A = B \quad K_A = Bx'$$

$$J_B = x' \quad K_B = A'x + Ax'$$

 

## 5.5 Analysis of clocked sequential circuits - Analysis with JK flip-flops

### State table and state diagram

**Table 5-4**

*State Table for Sequential Circuit with JK Flip-Flops*

Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 


Fig. 5-19 State Diagram of the Circuit of Fig. 5-18



## 5.5 Analysis of clocked sequential circuits - Analysis with T flip-flops

- Input equations and output equation


$$T_A = Bx, \quad T_B = x$$

$$y = AB$$

- State equations are derived from characteristic equation

$$A(t+1) = T_A A' + T_A' A$$

$$B(t+1) = T_B B' + T_B' B$$

 


(a) Circuit diagram

## 5.5 Analysis of clocked sequential circuits - Analysis with T flip-flops

**Table 5-5**

*State Table for Sequential Circuit with T Flip-Flops*

Present State		Input $x$	Next State		Output $y$
$A$	$B$		$A$	$B$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1


 


State/output

(b) State diagram Input
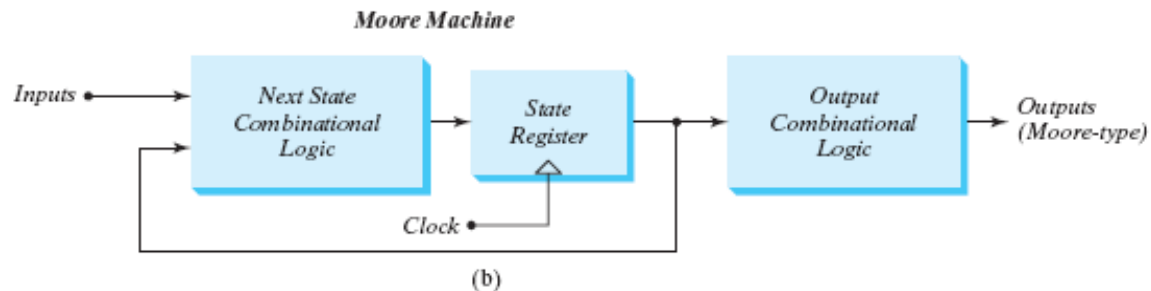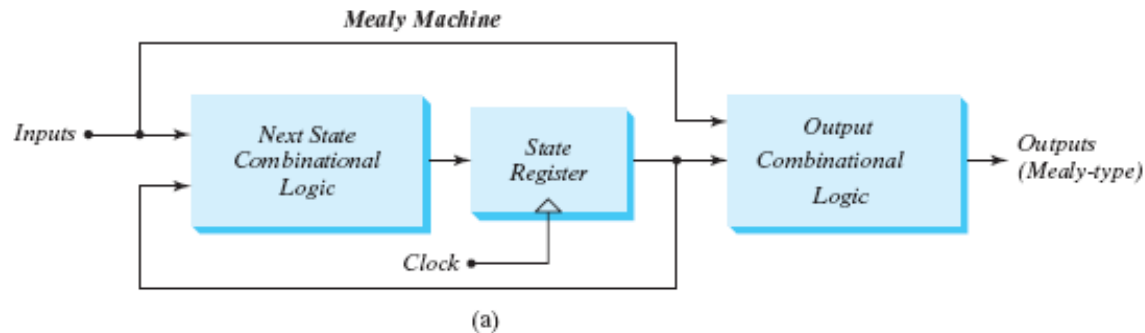
## 5.5 Analysis of clocked sequential circuits - Mealy and Moore models

- Mealy model : output is a function of the present state and input
- Inputs must be synchronized with the clock
- Outputs must be sampled at the clock edge
- Moore model : output is a function of the present state only
- Outputs are synchronized with the clock



## 5.7 State reduction and assignment

- State reduction is used to reduce the number of flip-flop
- Only input/output sequences are important
- Interested in present states that go to the same next state and have the same output

## 5.7 State reduction and assignment - State reduction

**Table 5-6**  
*State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

*Reducing the State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1

 


Fig. 5-22 State Diagram

## 5.7 State reduction and assignment - State reduction

**Table 5-8**  
*Reduced State Table*

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$a$	$a$	$b$	0	0
$b$	$c$	$d$	0	0
$c$	$a$	$d$	0	0
$d$	$e$	$d$	0	1
$e$	$a$	$d$	0	1

 


Fig. 5-23 Reduced State Diagram

## 5.7 State reduction and assignment - State assignment

- $m$  states circuit, codes must contain  $n$  bits where  $2^n \geq m$
- Three possible binary state assignments

**Table 5-9**  
*Three Possible Binary State Assignments*

State	Assignment 1 Binary	Assignment 2 Gray code	Assignment 3 One-hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

## 5.8 Design procedure

- Sequential circuit design : requires state table  
⇔ Combinational circuit : truth table
- The number of flip-flop is determined from the number of states in circuit
- If  $2^n$  states exist, there are  $n$  flip-flops



## 5.8 Design procedure

- Design steps

- 1) Derive a state diagram or state table
- 2) Reduce the number of states if necessary
- 3) Assign binary code to the state
- 4) Choose the type of flip-flops to be used
- 5) Derive the flip-flop input equations and output equations
- 6) Draw the logic diagram

## 5.8 Design procedure

- Derive a state diagram
  - Sequential detector
  - Three or more consecutive 1's in a string of bits coming through an input line

 


Fig. 5-24 State Diagram for Sequence Detector

## 5.8 Design procedure - Synthesis using D flip-flops

- Input equations are obtained directly from the next states


**Table 5.11**  
*State Table for Sequence Detector*

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1



## 5.8 Design procedure - Synthesis using D flip-flops

### ● Example waveform

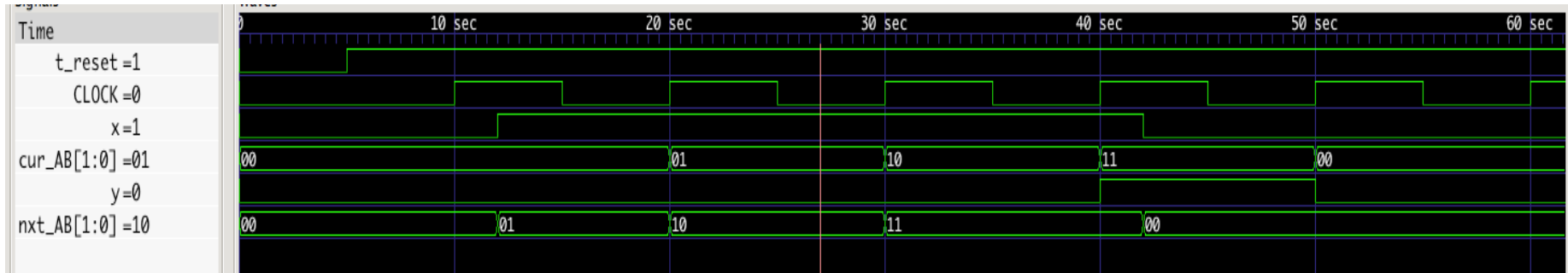

## 5.8 Design procedure - Synthesis using T flip-flops

- 3-bit binary counter
- 3-bit counter has 3 flip-flops and can count from 0 to  $2^n - 1$  ( $n=3$ )

 



Fig. 5-29 State Diagram of 3-Bit Binary Counter

## 5.8 Design procedure - Synthesis using T flip-flops


### State table and logic diagram

**Table 5-14**  
*State Table for 3-Bit Counter*


Present State			Next State			Flip-Flop Inputs		
$A_2$	$A_1$	$A_0$	$A_2$	$A_1$	$A_0$	$T_{A2}$	$T_{A1}$	$T_{A0}$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

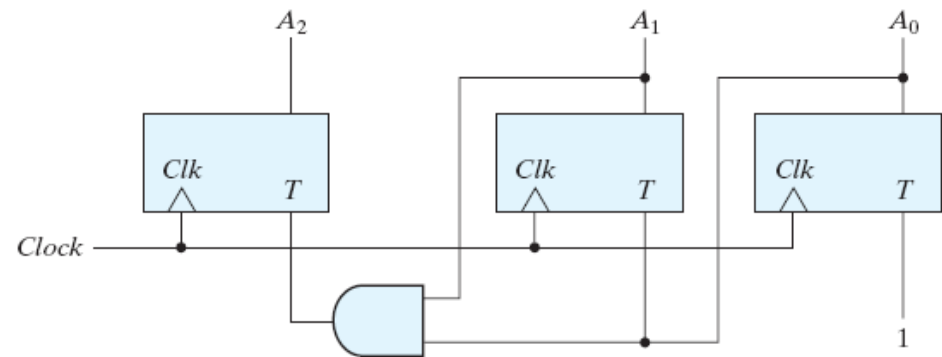

 
$$T_{A2}=A_1A_0, \quad T_{A1}=A_0, \quad T_{A0}=1$$



$$T_{A2} = A_1A_0$$

 

$$T_{A1} = A_0$$

 

$$T_{A0} = 1$$