

3. Gate-Level Minimization

3.1 Introduction

- The complexity of digital logic gates that implement a Boolean function
 - directly related to the function expression
- So, we want to find the simplest possible expression of a given function
- Method based on **Truth Table**
 - K-map (Karnaugh map)

3.2 The Map Method

Two-Variable Map

 


Fig. 3-1 Two-variable Map

● $m_1 + m_2 + m_3 = x'y + xy' + xy = x + y$

 


Fig. 3-2 Representation of Functions in the Map

Three-Variable Map (Careful! bit sequence is Gray-coded – adjacent entries differ by only one bit)

 


FIGURE 3.3
Three-variable K-map

3.2 The Map Method

- Ex 3-1) Simplify the Boolean function, $F(x, y, z) = \Sigma(2, 3, 4, 5)$

$$F = x'y + xy'$$

		yz		y	
x		00	01	11	10
x	0			1	1
	1	1	1		

z

Fig. 3-4 Map for Example 3-1; $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

- Ex 3-4) Given Boolean function, $F = A'C + A'B + AB'C + BC$

a) express it in sum of minterms

$$F(x, y, z) = \Sigma(1, 2, 3, 5, 7)$$

b) find the minimal sum of products

$$F = C + A'B$$

		BC		B	
A		00	01	11	10
A	0		1	1	1
	1		1	1	

C


Fig. 3-7 Map for Example 3-4; $A'C + A'B + AB'C + BC = C + A'B$

- Find the largest possible rectangle – size 1,2,4,8,16
- Find the expressions to represent the outputs of the rectangle

3.2 The Map Method

- Simplify the Boolean function, $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$

$$F = z' + xy'$$

 


Note: $y'z' + yz' = z'$

- Simplify

$$F(x, y, z) = \Sigma(3, 4, 6, 7)$$

$$F = yz + xz'$$

 

Note: $xy'z' + xyz' = xz'$

3.3 Four-Variable Map

 


Fig. 3-8 Four-variable Map

Ex 3-5) Simplify the Boolean function,

$$F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

$$F = y' + w'z' + xz'$$

 


Fig. 3-9 Map for Example 3-5; $F(w, x, y, z)$

$$= \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$$

3.3 Four-Variable Map – Prime Implicants

● $F(A,B,C,D) = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$

		CD		C	
AB		00	01	11	10
A	00	1		1	1
	01		1	1	
	11		1	1	
	10	1	1	1	1

D

B

- Prime implicant: the largest rectangles, can be of size 1,2,4,8 or 16.
- Essential prime implicant: prime implicant which contains a square which is not covered by other implicants

3.3 Four-Variable Map – Prime Implicants

● $F(A,B,C,D) = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$

		CD		C	
AB		00	01	11	10
A	00	1		1	1
	01		1	1	
	11		1	1	
	10	1	1	1	1

B is indicated by a bracket on the right side of the rows.

D is indicated by a bracket below the columns.

- There are 5 prime implicants
- there are 2 essential prime implicants

3.3 Four-Variable Map – Prime Implicants

● $F(A,B,C,D) = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$


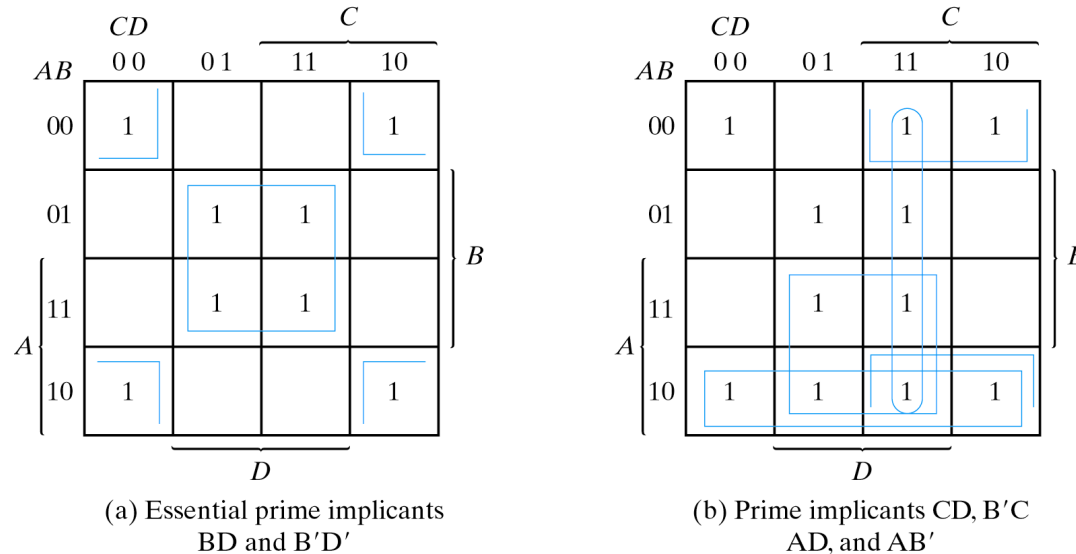


Fig. 3-11 Simplification Using Prime Implicants


- Procedure:
 1. Find essential prime implicants, and derive corresponding minterms
 2. Find other prime implicants which contain uncovered squares in Step 1, and derive minterms

 3.3 Four-Variable Map – Prime Implicants

● $F(A,B,C,D) = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$



 (a) Essential prime implicants
BD and $B'D'$



(b) Prime implicants CD, $B'C$
AD, and AB'

Fig. 3-11 Simplification Using Prime Implicants

$$\begin{aligned}
 F &= BD + B'D' + CD + AD \\
 &= BD + B'D' + CD + AB' \\
 &= BD + B'D' + B'C + AD \\
 &= BD + B'D' + CD + AB'
 \end{aligned}$$

3.4 Five-Variable Map (NOT COVERED)

$A = 0$

		DE		D	
		00	01	11	10
BC	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

E

$A = 1$

		DE		D	
		00	01	11	10
BC	00	16	17	19	18
	01	20	21	23	22
	11	28	29	31	30
	10	24	25	27	26

E

Fig. 3-12 Five-variable Map

Table 3-1

The Relationship Between the Number of Adjacent Squares and the Number of Literals In the Term

K	Number of Adjacent Squares 2^k	Number of Literals in a Term in an n -variable Map			
		$n = 2$	$n = 3$	$n = 4$	$n = 5$
0	1	2	3	4	5
1	2	1	2	3	4
2	4	0	1	2	3
3	8		0	1	2
4	16			0	1
5	32				0

3.4 Five-Variable Map (NOT COVERED)

- Ex 3-7) Simplify the Boolean function,
 $F(A,B,C,D,E) = \Sigma(0,2,4,6,9,13,21,23,25,29,31)$

 


Fig. 3-13 Map for Example 3-7; $F = A'B'E' + BD'E + ACE$

3.5 Product of Sums Simplification

- Ex 3-8) Simplify the Boolean function,
 $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 7, 9, 10)$

a) sum of products

$$F = B'D' + B'D' + A'C'D'$$


b) product of sum

$$F' = AB + CD + BD' \text{ (use K-map for 0 entries)}$$


$$F = (A' + B')(C' + D')(B' + D) \text{ (deMorgan's law)}$$

		CD		C	
		00	01	11	10
AB	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1

Fig. 3-14 Map for Example 3-8; $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 7, 9, 10)$
 $= B'D' + B'C' + A'C'D = (A' + B')(C' + D')(B' + D)$

 

(a) $F = B'D' + B'C' + A'C'D$

 

(b) $F = (A' + B')(C' + D')(B' + D)$

Fig. 3-15 Gate Implementation of the Function of Example 3-8

3.5 Product of Sums Simplification

Table 3-2
Truth Table of Function F

<i>x</i>	<i>y</i>	<i>z</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		<i>yz</i>		<i>y</i>	
		00	01	11	10
<i>x</i>	0	0	1	1	0
	1	1	0	0	1
		<i>z</i>			

Fig. 3-16 Map for the Function of Table 3-2

• $F(x, y, z) = \Sigma(1, 3, 4, 6) = \Pi(0, 2, 5, 7)$

$$F = x'z + xz'$$

$$F' = xz + x'z'$$

$$F = (x' + z)(x + z')$$

3.6 Don't-Care Conditions (NOT COVERED)

- Ex 3-9) Simplify the Boolean function, $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$
Don't-care conditions, $d(w, x, y, z) = \Sigma(0, 2, 5)$

		yz		y		
		00	01	11	10	
wx						
00		X	1	1	X	x
01		0	X	1	0	
11	w	0	0	1	0	
10		0	0	1	0	
		z				

(a) $F = yz + w'x'$

		yz		y		
		00	01	11	10	
wx						
00		X	1	1	X	} x
01		0	X	1	0	
11	} w	0	0	1	0	
10		0	0	1	0	
		} z				

(a) $F = yz + w'z$

Fig. 3-17 Example with don't-care Conditions

$$F(w, x, y, z) = yz + w'x' = \Sigma(0, 1, 2, 3, 7, 11, 15)$$

$$F(w, x, y, z) = yz + w'z = \Sigma(1, 3, 5, 7, 11, 15)$$

3.7 NAND and NOR Implementation – NAND Circuit

 


Fig. 3-18 Logic Operations with NAND Gates


 



Fig. 3-19 Two Graphic Symbols for NAND Gate

3.7 NAND and NOR Implementation – Two Level Implementation


• $F = ((AB)'(CD)')' = AB + CD$

 

(a)

 

(b)

 


(c)

Fig. 3-20 Three Ways to Implement $F = AB + CD$


- Ex 3-10) Implement the following Boolean function with NAND gates:

$$F(x, y, z) = \Sigma(1, 2, 3, 4, 5, 7) = xy' + x'y + z$$

		y			
		yz			
		00	01	11	10
x	0		1	1	1
x	1	1	1	1	

 


(b)

 


(c)

Fig. 3-21 Solution to Example 3-10

 3.7 NAND and NOR Implementation – Multilevel NAND Circuit



(a) AND-OR gates

 

(a) NAND gates

Fig. 3-22 Implementing $F = A(CD + B) + BC$

3.7 NAND and NOR Implementation – NOR Implementation

NOR Implementation



 


Fig. 3-24 Logic Operations with NOR Gates

 

(a) OR–invert

 

(a) Invert–AND

Fig. 3-25 Two Graphic Symbols for NOR Gate

$$F = (AB' + A'B)(C + D')$$


 



Fig. 3-27 Implementing $F = (AB' + A'B)(C + D')$ with NOR Gates

3.8 Other Two-Level Implementation

 - (a) $F = (AB)' \cdot (CD)' = (AB + CD)'$
- (b) $F = (A + B)' + (C + D)' = [(A + B)(C + D)]'$



 (a) Wired-AND in open-collector
TTL NAND gates.
(AND-OR-INVERT)




(b) Wired-OR in ECL gates
(OR-AND-INVERT)


3.8 Other Two-Level Implementation

● AND-OR-Invert Circuits


$$F = (AB + CD + E)'$$

 

(a) AND-NOR

 

(b) AND-NOR

 


(c) NAND-AND


3.8 Other Two-Level Implementation

OR-AND-Invert Circuits


$$F = [(A + B)(C + D)E]'$$

 

(a) OR-NAND

 

(b) OR-NAND

 

(c) NOR-OR

3.8 Other Two-Level Implementation

Table 3.3
Implementation with Other Two-Level Forms

Equivalent Nondegenerate Form		Implements the Function	Simplify F' into	To Get an Output of
(a)	(b)*			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	F
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	F

*Form (b) requires an inverter for a single literal term.

3.9 Exclusive-OR Function

- $x \oplus y = xy' + x'y$

$$(x \oplus y)' = (xy' + x'y)' = xy + x'y'$$

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$


$$x \oplus x = 0$$

$$x \oplus x' = 1$$


$$x \oplus y' = x' \oplus y = (x \oplus y)'$$

- $A \oplus B = B \oplus A$
 
$$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$



(a) With AND-OR-NOT gates

 

(b) With NAND gates

Fig. 3-32 Exclusive-OR Implementations

3.9 Exclusive-OR Function


● Odd / Even Function

A \ BC	B			
	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_4	m_5	m_7	m_6


(a) Odd function $F = A \oplus B \oplus C$

A \ BC	B			
	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_4	m_5	m_7	m_6

 (b) Even function $F = (A \oplus B \oplus C)'$



(a) 3-input odd function

 

(b) 3-input even function


3.9 Exclusive-OR Function - Parity Generation and Checking

● Parity Generation and Checking

Table 3-4
Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$P = x \oplus y \oplus z$$

 


(a) 3-bit even parity generator

Table 3-5
Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$C = x \oplus y \oplus z \oplus P$$

 

(a) 4-bit even parity checker

Fig. 3-36 Logic Diagram of a Parity Generator and Checker