

## Ch 4. Combinational logic

## 4.2 Combinational circuits

- Outputs are determined from the present inputs
- Consist of input/output variables and logic gates

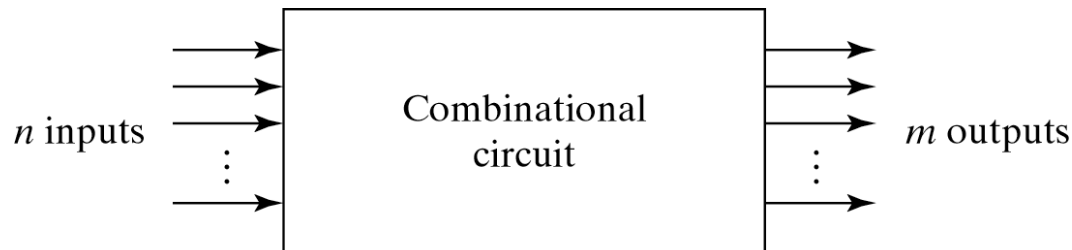


Fig. 4-1 Block Diagram of Combinational Circuit

## 4.3 Analysis procedure

- To determine the function of circuit
- Analysis procedure
  - Make sure the circuit is combinational or sequential
  - Obtain the output Boolean functions or the truth table

## 4.3 Analysis procedure

- Boolean function
  - Label all gate outputs
  - Make output functions at each level
  - Substitute final outputs to input variables
- Truth table
  - Put the input variables to binary numbers
  - Determine the output value at each gate
  - Obtain truth table

## 4.3 Analysis procedure

**Table 4-1**  
Truth Table for the Logic Diagram of Fig. 4-2

A	B	C	$F_2$	$F_2$	$T_1$	$T_2$	$T_3$	$F_1$
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

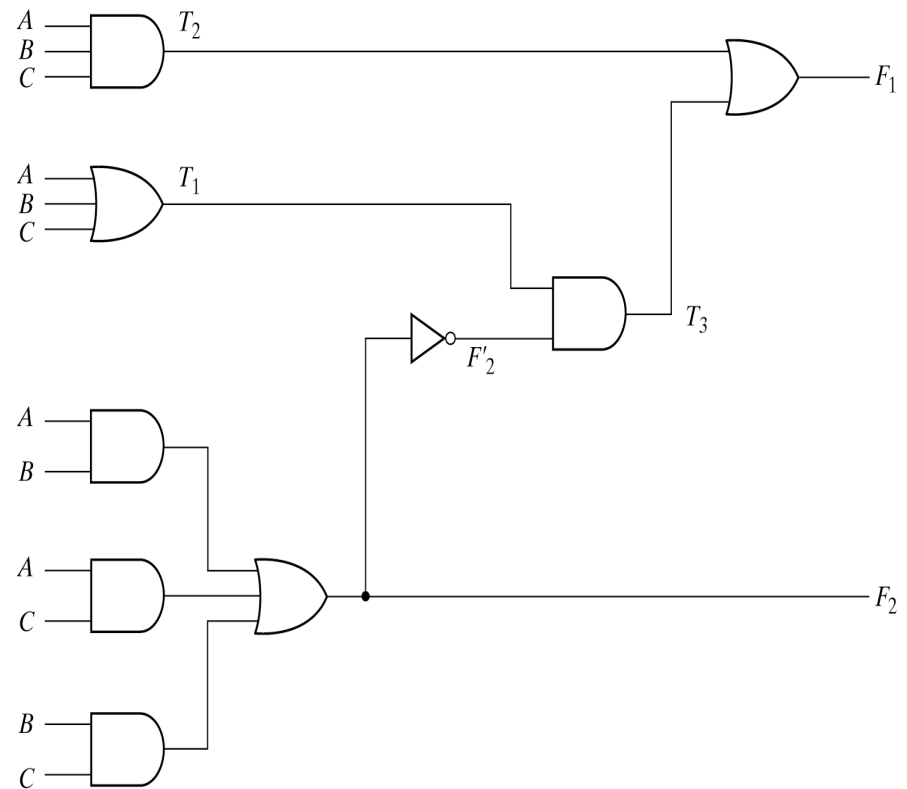


Fig. 4-2 Logic Diagram for Analysis Example

## 4.4 Design procedure

- Procedure to design
  - Determine the required number of input and output from specification
  - Assign a letter symbol to each input/output
  - Derive the truth table
  - Obtain the simplified Boolean functions
  - Draw the logic diagram and verify design correctness

## 4.5 Binary adder-subtractor

- Binary adder
  - Half adder : performs the addition of 2-bits( $x+y$ )
  - Full adder : performs the addition of 3-bits( $x+y+z$ )
  - Two half adder can be employed to a full adder
- Realization of Binary adder-subtractor
  - Half adder
  - Full adder
  - Cascade of  $n$ -full adder
  - Providing a complementing circuit

## 4.5 Binary adder-subtractor - Half Adder

### • Sum of 2 binary inputs

1. Determine # of input & outputs
  - 2-bit input, 2-bit output

• Input : X(augend), Y(addend) 2. assign variables  
Output : S(sum), C(carry)

3. draw truth table 4. simplify logic if possible

**Table 4-3**  
*Half Adder*


<i>x</i>	<i>y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = xy' + x'y$$


$$C = xy$$


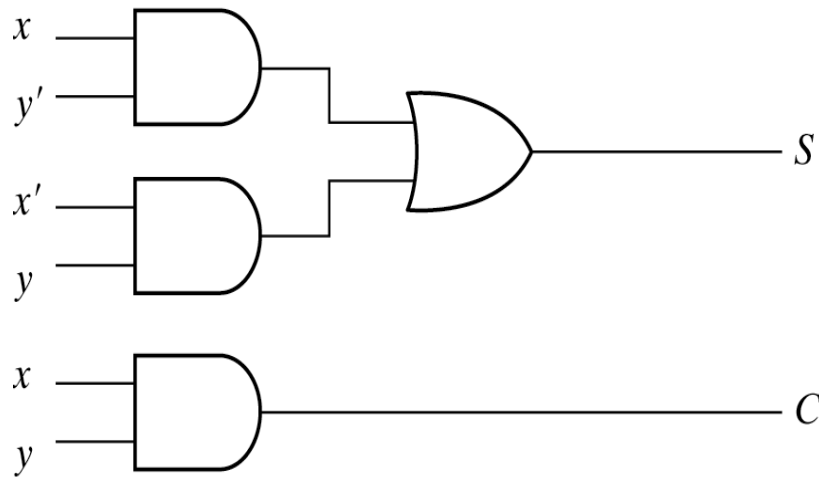
## 4.5 Binary adder-subtractor - Half Adder


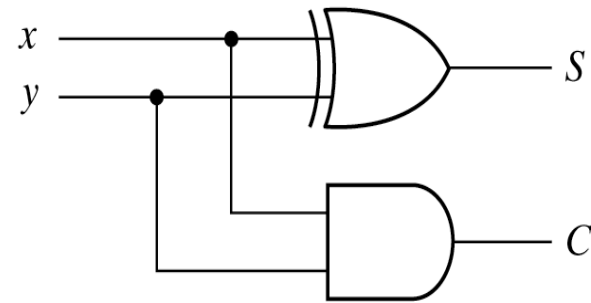
$$(a) \begin{aligned} S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$(b) \begin{aligned} S &= x \oplus y \\ C &= xy \end{aligned}$$

Fig. 4-5 Implementation of Half-Adder

## 4.5 Binary adder-subtractor - Full adder

- Sum of 3 binary inputs
- Input : X,Y(2 significant bits),Z(1 carry bit)
- Output : S(sum),C(carry)

**Table 4-4**  
*Full Adder*

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

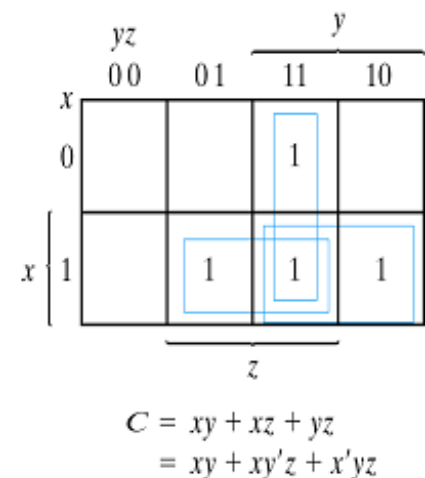
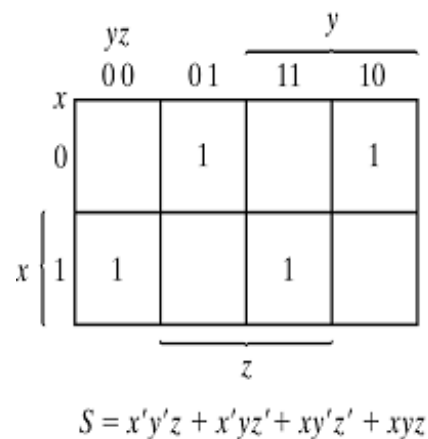


Fig. 4-6 Maps for Full Adder

## 4.5 Binary adder-subtractor - Full adder

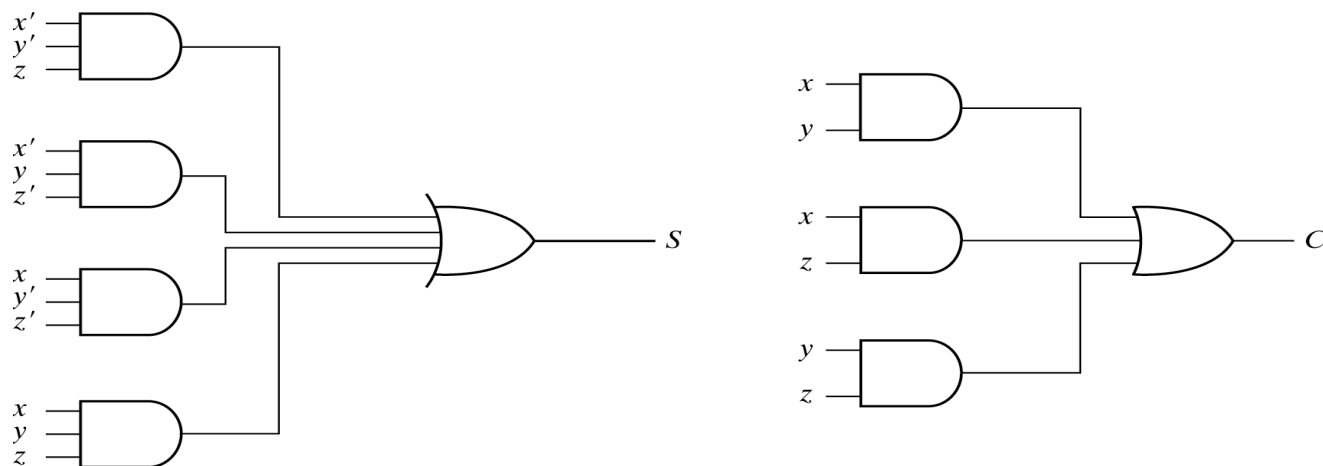


Fig. 4-7 Implementation of Full Adder in Sum of Products

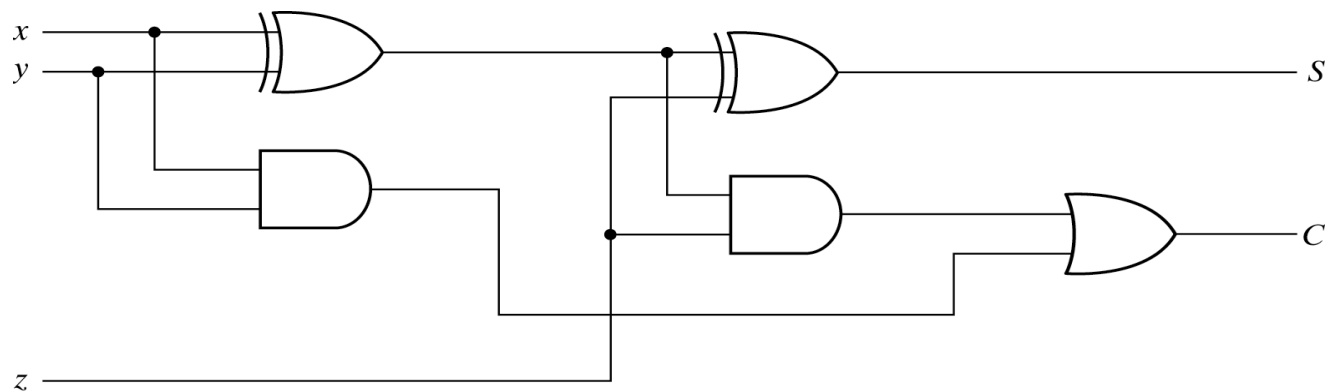


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

## 4.5 Binary adder-subtractor - Binary adder

### ● Sum of two n-bit binary numbers

#### – 4-bit adder

A=1011, B=0011

<i>Subscript i:</i>	<b>3</b>	<b>2</b>	<b>1</b>	<b>0</b>	
Input carry	0	1	1	0	$C_i$
Augend	1	0	1	1	$A_i$
Addend	0	0	1	1	$B_i$
Sum	1	1	1	0	$S_i$
Output carry	0	0	1	1	$C_{i+1}$

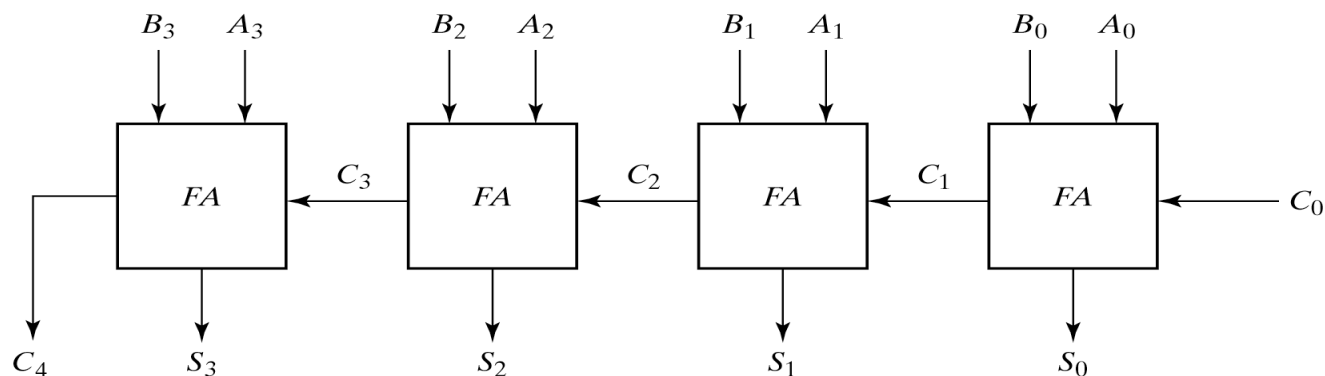


Fig. 4-9 4-Bit Adder

## 4.5 Binary adder-subtractor - Carry propagation

- Rising of delay time(carry delay)
- One solution is **carry lookahead**
- All carry is a function of  $P_i, G_i$  and  $C_0$

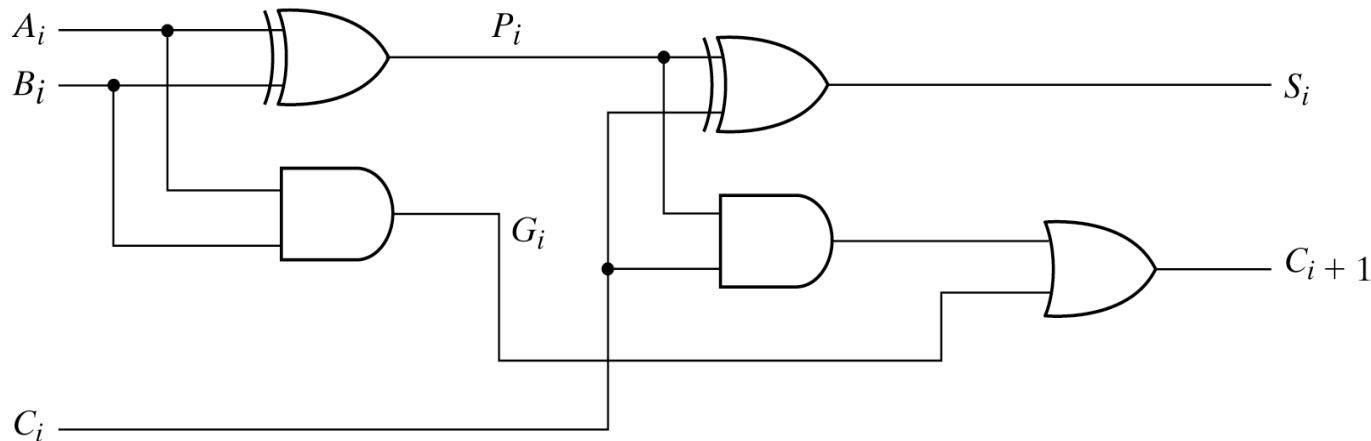


Fig. 4-10 Full Adder with P and G Shown

$$\begin{aligned} C_{i+1} &= G_i + P_i C_i \\ S_i &= P_i \oplus C_i \end{aligned}$$

## 4.5 Binary adder-subtractor - Carry propagation

### ● Carry lookahead generator

$C_0$  = input carry

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1 = G_1 + P_1(G_0 + P_0C_0) = G_1 + P_1G_0 + P_1P_0C_0$$

$$C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

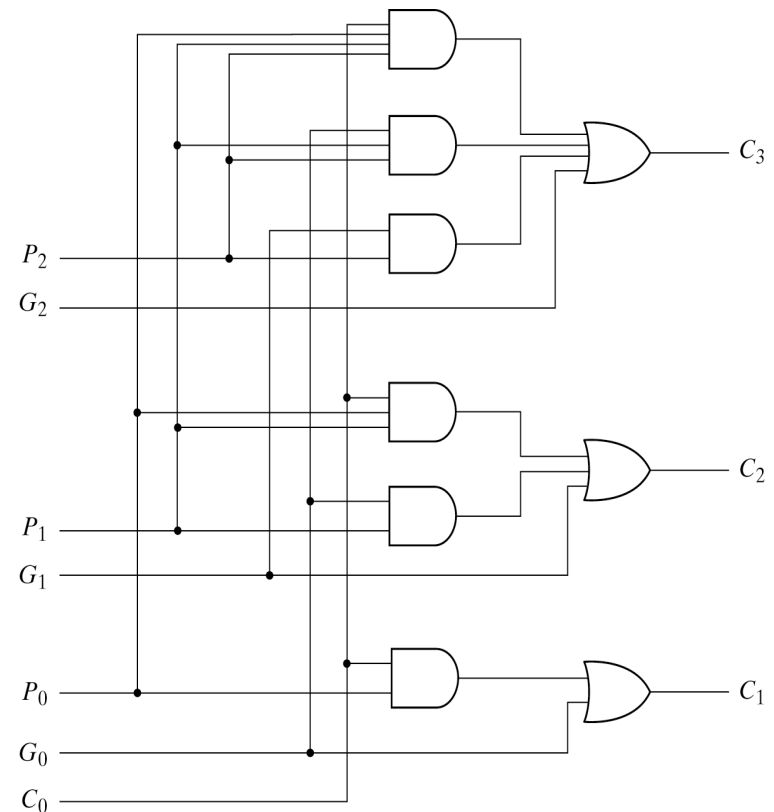


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

## 4.5 Binary adder-subtractor - Carry propagation

### 4-bit adder with carry lookahead

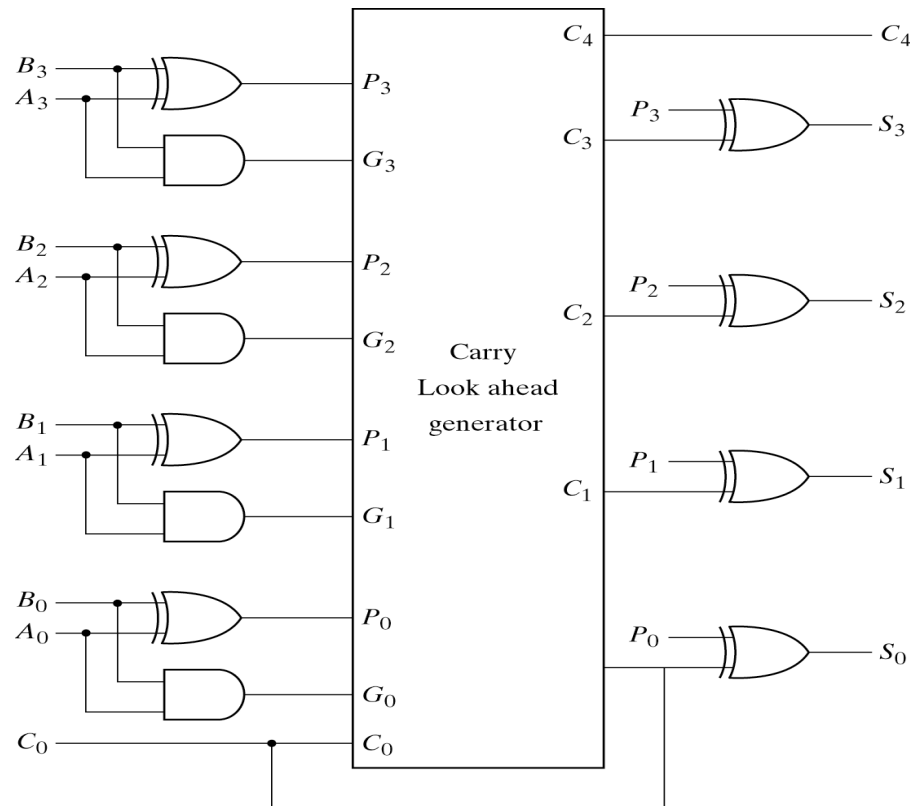


Fig. 4-12 4-Bit Adder with Carry Lookahead

## 4.5 Binary adder-subtractor - Binary subtractor

- $A - B$  equals  $A + (2' \text{ complement of } B)$
- When  $M=0$  (act as adder)  $M=1$  (subtractor)

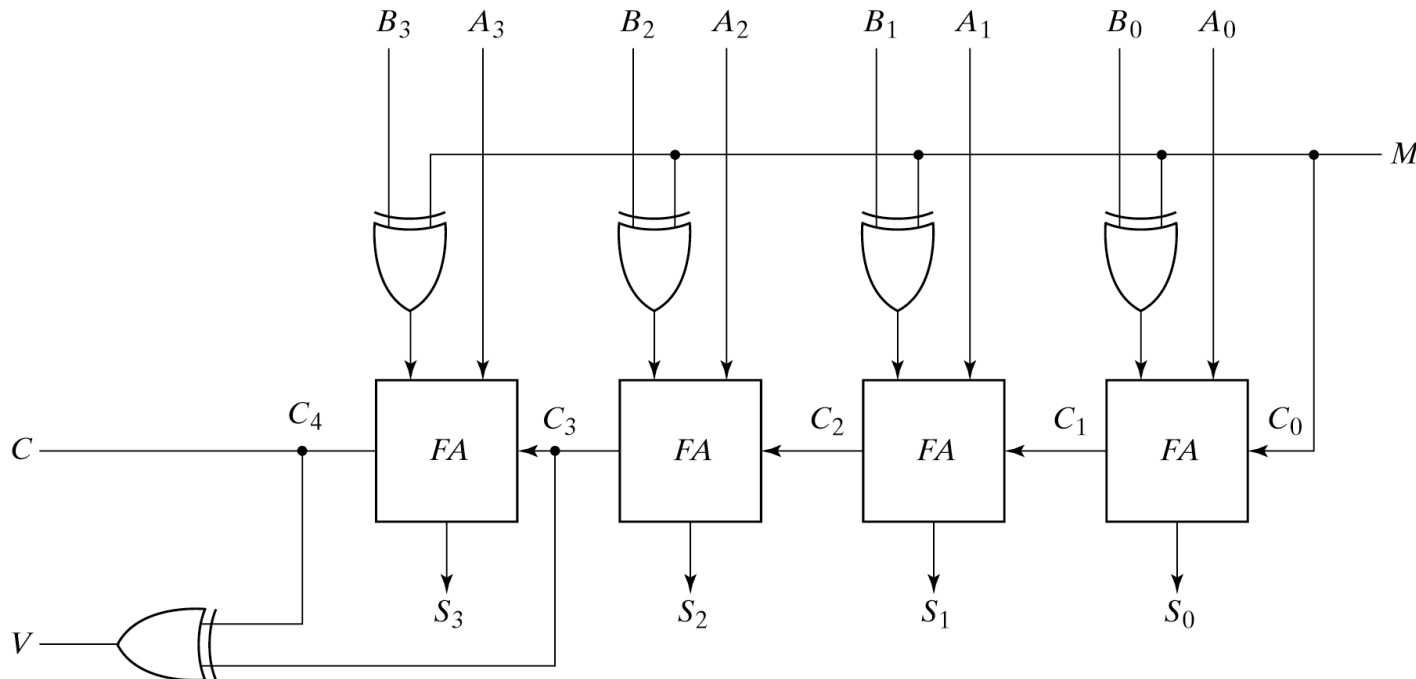


Fig. 4-13 4-Bit Adder Subtractor



## 4.5 Binary adder-subtractor - Overflow

- Sum of  $n$  digit number occupies  $n+1$  digit
- Occurs when two numbers are same sign

(examples of overflow)

carries: 0 1

+70	0	1000110
+80	0	1010000
<hr/>		
+150	1	0010110

carries: 1 0

-70	1	0111010
-80	1	0110000
<hr/>		
-150	0	1101010

## 4.6 Decimal adder

- Calculate binary and represent decimal in binary coded form
- Decimal adder for the BCD code

**Table 4.5**  
*Derivation of BCD Adder*

<i>K</i>	Binary Sum				BCD Sum					Decimal
	<i>Z</i> <sub>8</sub>	<i>Z</i> <sub>4</sub>	<i>Z</i> <sub>2</sub>	<i>Z</i> <sub>1</sub>	<i>C</i>	<i>S</i> <sub>8</sub>	<i>S</i> <sub>4</sub>	<i>S</i> <sub>2</sub>	<i>S</i> <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

## 4.6 Decimal adder - BCD Adder

- BCD digit output of 2-B CD digit sum
- Carry arise if output 1010~1111
- $C = K + Z_8Z_4 + Z_8Z_2$

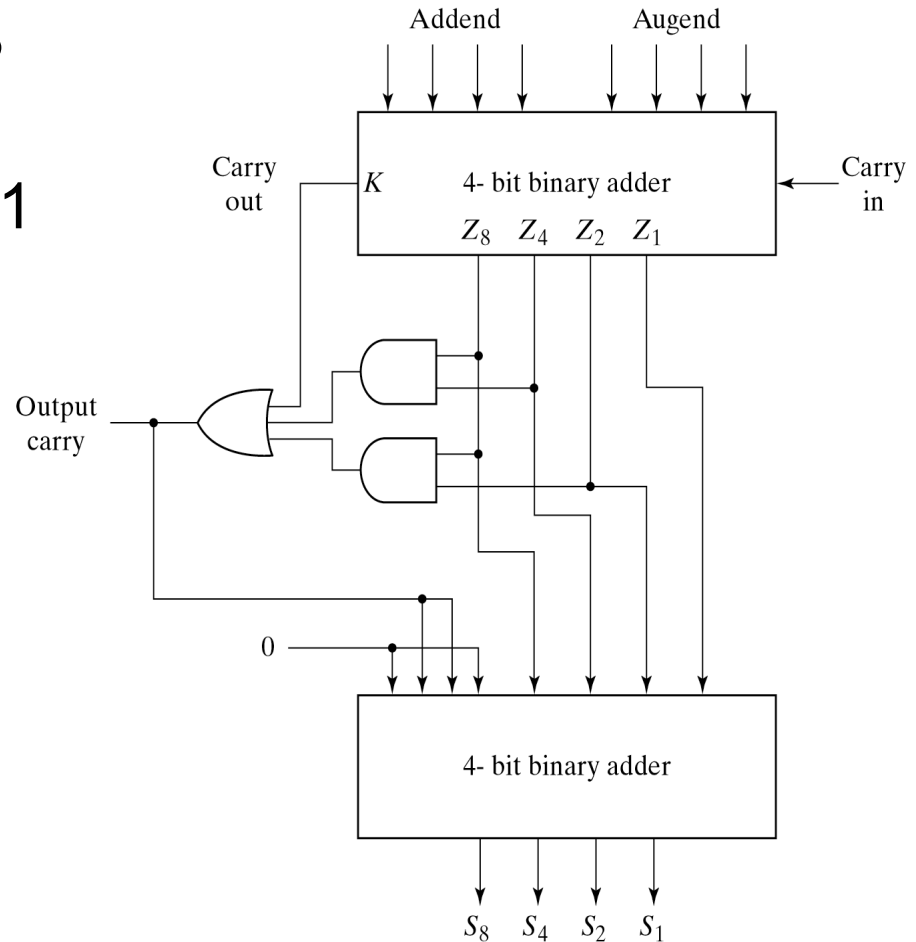
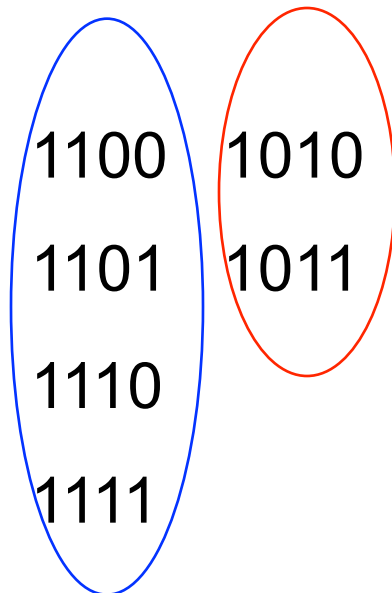


Fig. 4-14 Block Diagram of a BCD Adder

## 4.7 Binary multiplier

- 2bit x 2bit = 4bit(max)

		$B_1$	$B_0$
	$A_1$	$A_1B_1$	$A_1B_0$
	$A_0$	$A_0B_1$	$A_0B_0$
$C_3$	$C_2$	$C_1$	$C_0$

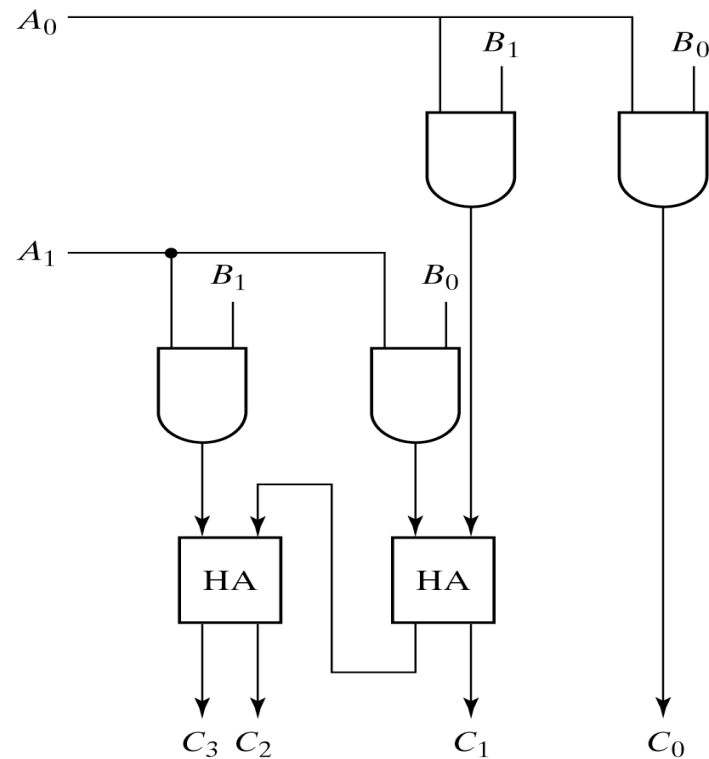


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

## 4.7 Binary multiplier

- (K-bit) x (J-bit)
  - (K x J) AND gates,
  - (J-1) K-bit adder needed

$$\begin{array}{r} B_3 B_2 B_1 B_0 \\ \times \quad A_2 A_1 A_0 \\ \hline \end{array}$$

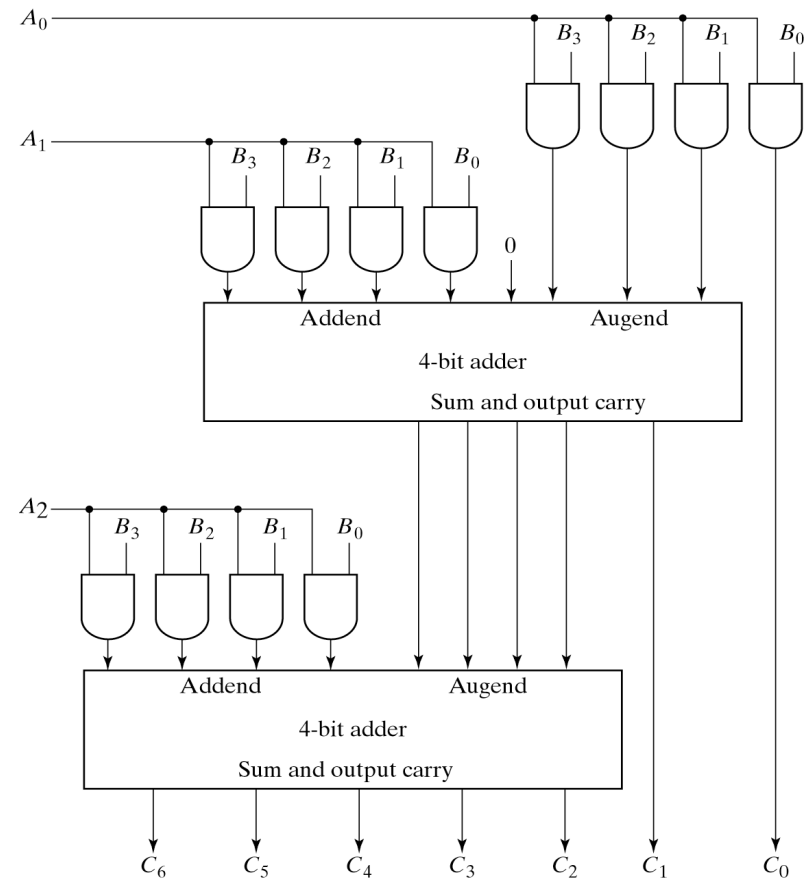


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

## 4.8 Magnitude comparator

- $X_i=1$  only if the pair of bits  $i$  in  $A$  and  $B$  are equal
- $(A=B)=X_3X_2X_1X_0$
- $(A>B)=A_3B_3'+x_3A_2B_2'+x_3x_2A_1B_1'+x_3x_2x_1A_0B_0'$
- $(A<B)=A_3'B_3+x_3A_2'B_2+x_3x_2A_1'B_1+x_3x_2x_1A_0'B_0$

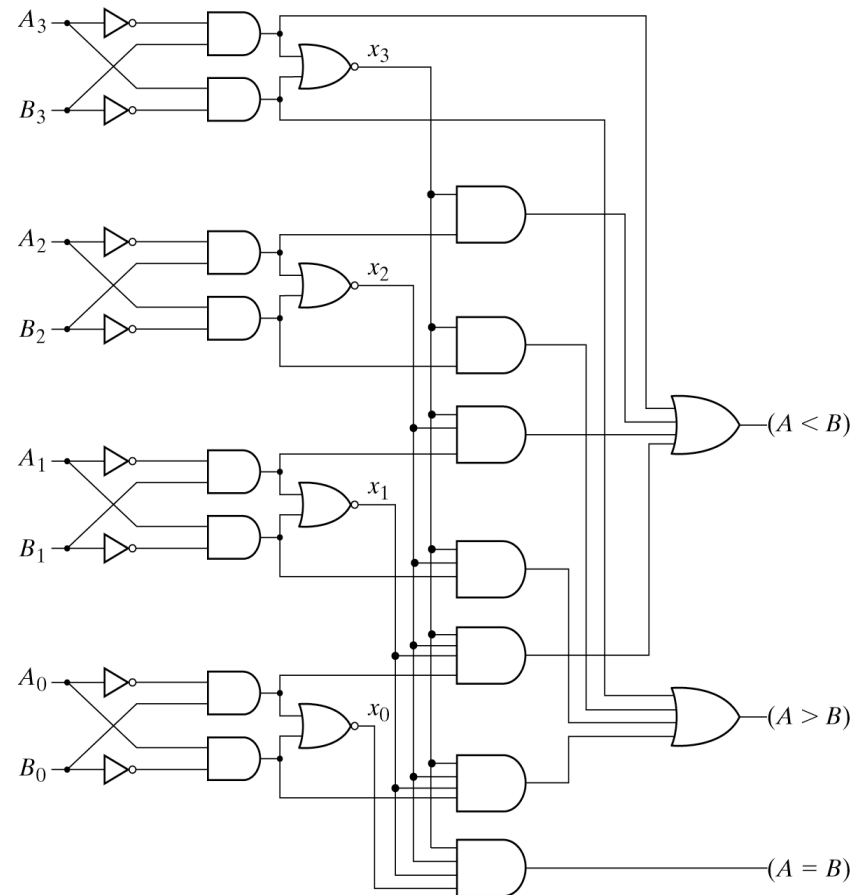


Fig. 4-17 4-Bit Magnitude Comparator

## 4.9 Decoders

- Generate the  $2^n$ (or less) minterms of  $n$  input variables
  - Eg) 3 to 8 line decoder

**Table 4-6**  
*Truth Table of a 3-to-8-Line Decoder*

Inputs			Outputs							
$x$	$y$	$z$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


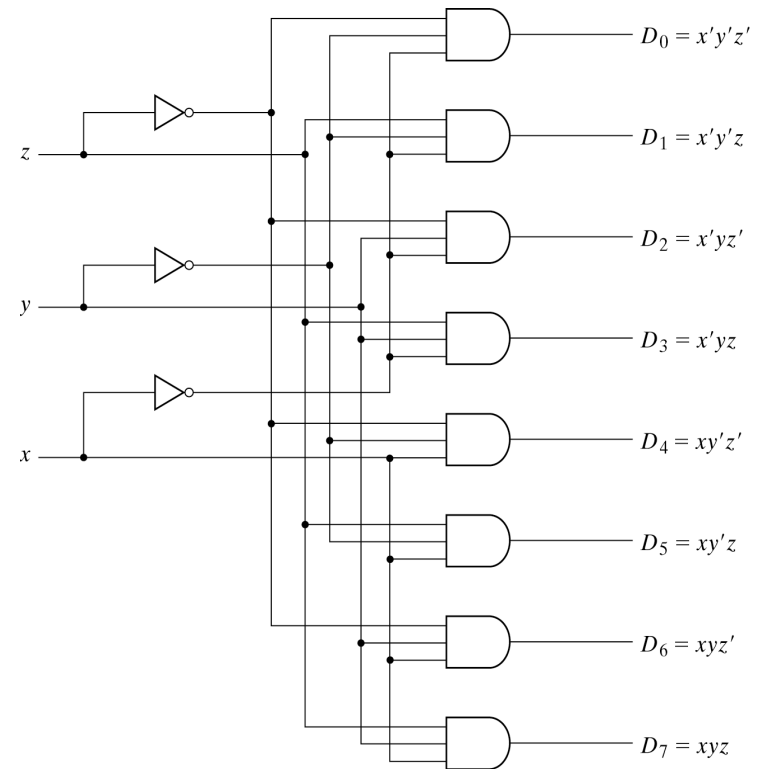


Fig. 4-18 3-to-8-Line Decoder
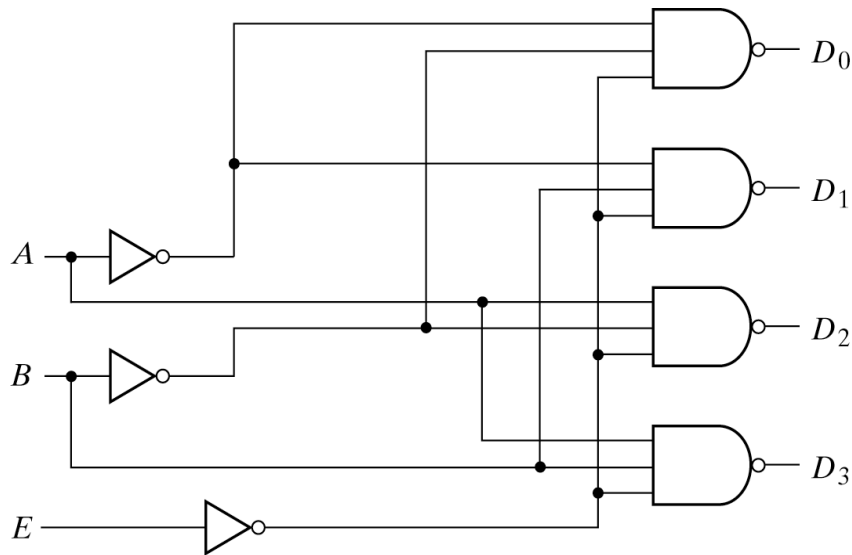
## 4.9 Decoders

- 2 to 4 line decoder with Enable input
  - Control circuit operation by E



(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>
1	<i>X</i>	<i>X</i>	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input



## 4.9 Decoders

- Decoders with enable inputs can be a larger decoder circuit

Eg) 4x16 decoder by two 3x8 decoders

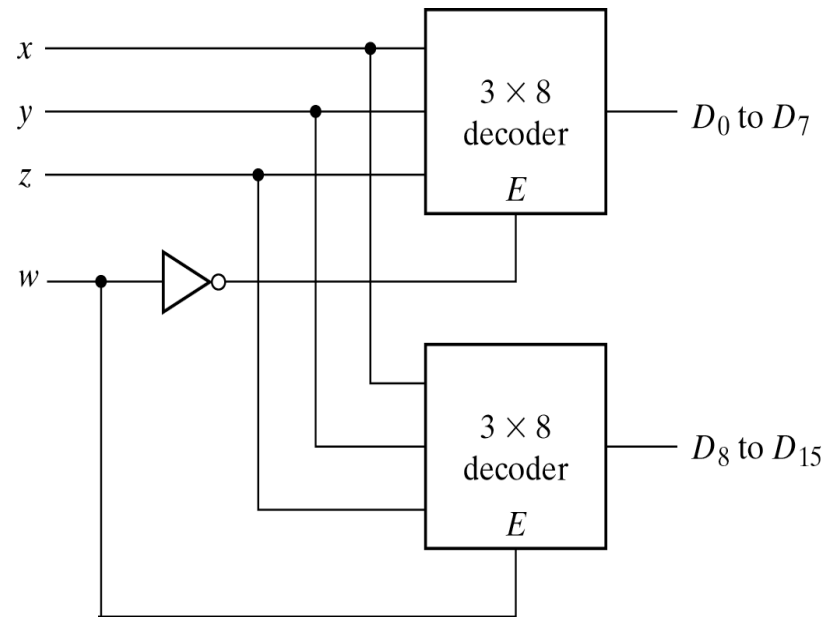


Fig. 4-20  $4 \times 16$  Decoder Constructed with Two  $3 \times 8$  Decoders

## 4.9 Decoders - Combinational logic implementation

- Combinational logic implementation
  - Any combinational circuit can be implemented with line decoder and OR gates
  - Eg) full adder

**Table 4-4**  
*Full Adder*

$x$	$y$	$z$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

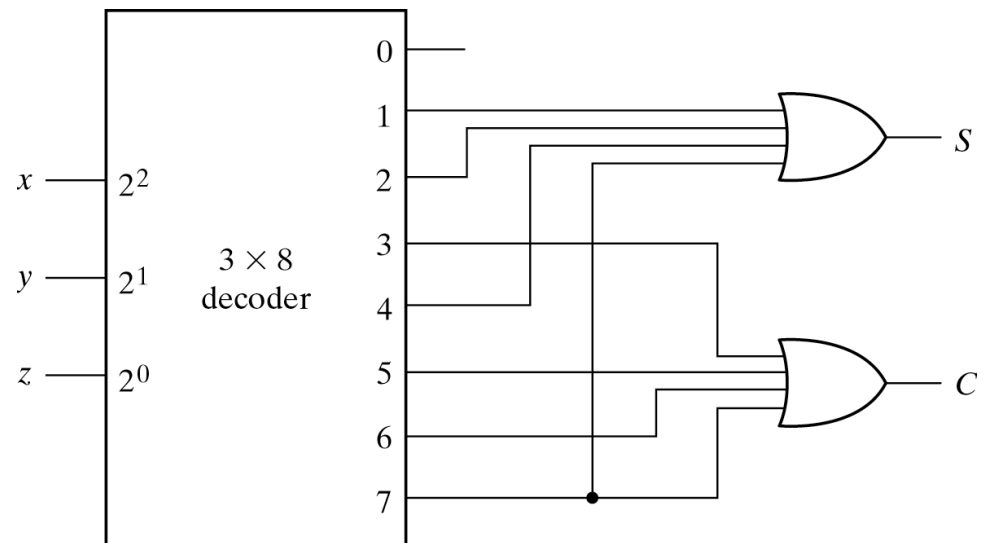


Fig. 4-21 Implementation of a Full Adder with a Decoder

## 4.10 Encoders

- Inverse operation of a decoder
- Generate  $n$  outputs of  $2^n$  input values
  - Eg) octal to binary encoder

**Table 4-7**  
*Truth Table of Octal-to-Binary Encoder*

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

## 4.10 Encoders - Priority encoder

- Problem happens two or more inputs equal to 1 at the same time
- Give a priority function to circuit

Table 4-8  
Truth Table of a Priority Encoder

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	$X$	$X$	0
1	0	0	0	0	0	1
$X$	1	0	0	0	1	1
$X$	$X$	1	0	1	0	1
$X$	$X$	$X$	1	1	1	1

(x100 means 0100, 1100)

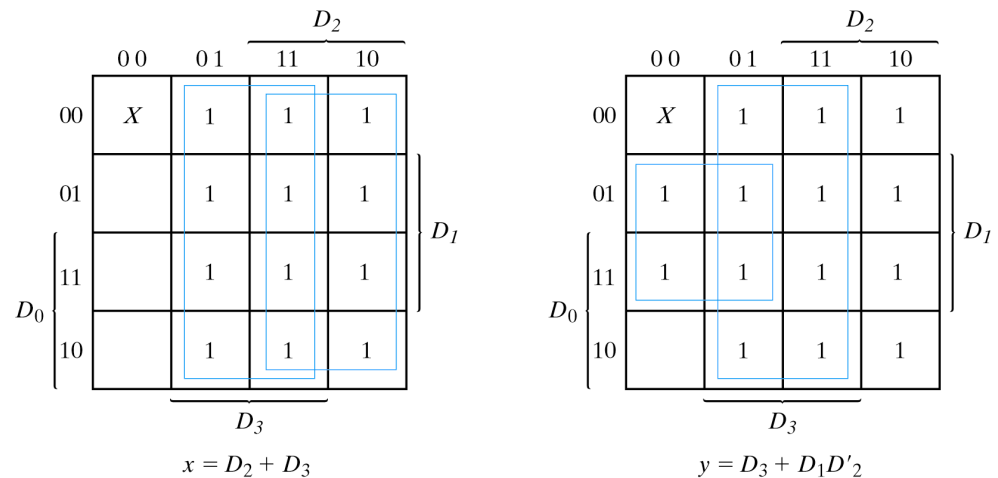


Fig. 4-22 Maps for a Priority Encoder

## 4.11 Multiplexers


- Select a binary information from many input lines
- Selection is controlled by a set of selection lines
- $2^n$  input lines have  $n$  selection lines

## 4.11 Multiplexers

### 4 to 1 line multiplexer

$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

(b) Function table

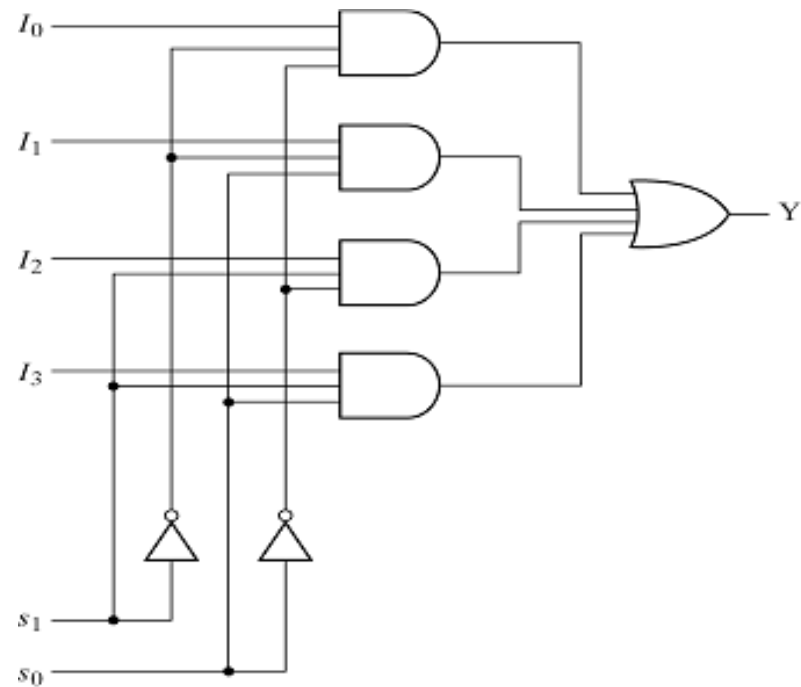

(a) Logic diagram

## 4.11 Multiplexers

### • Quadruple 2 to 1 line multiplexer

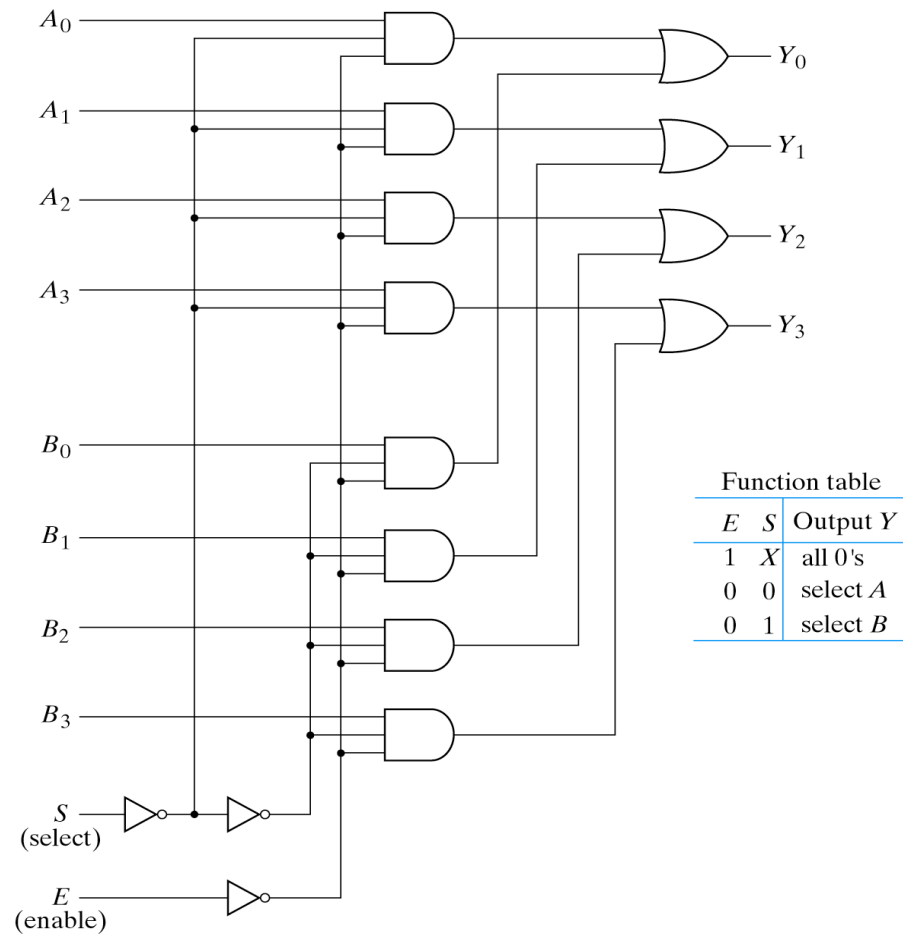



Fig. 4-26 Quadruple 2-to-1-Line Multiplexer

## 4.11 Multiplexers - Boolean function implementation

- Boolean function implementation
  - Minterms of function are generated in a MUX
  - $n$  input variables,  $n-1$  selection input

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a) Truth table

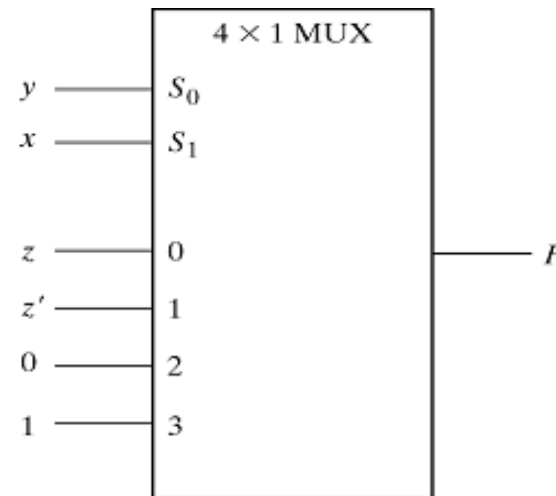

(b) Multiplexer implementation

$$F = xy + yz' + x'y'z$$



## 4.11 Multiplexers - Three-state gates

- Three-state gates
  - Logic 1, 0 and *high-impedance*
  - *High-impedance* behaves like an open circuit

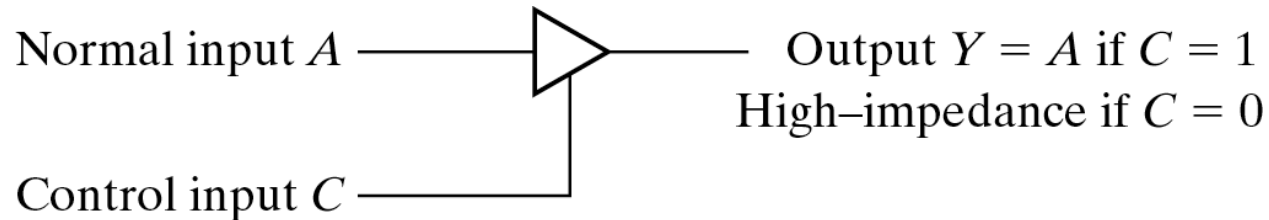


Fig. 4-29 Graphic Symbol for a Three-State Buffer

## 4.11 Multiplexers

### • Multiplexers with three-state gates

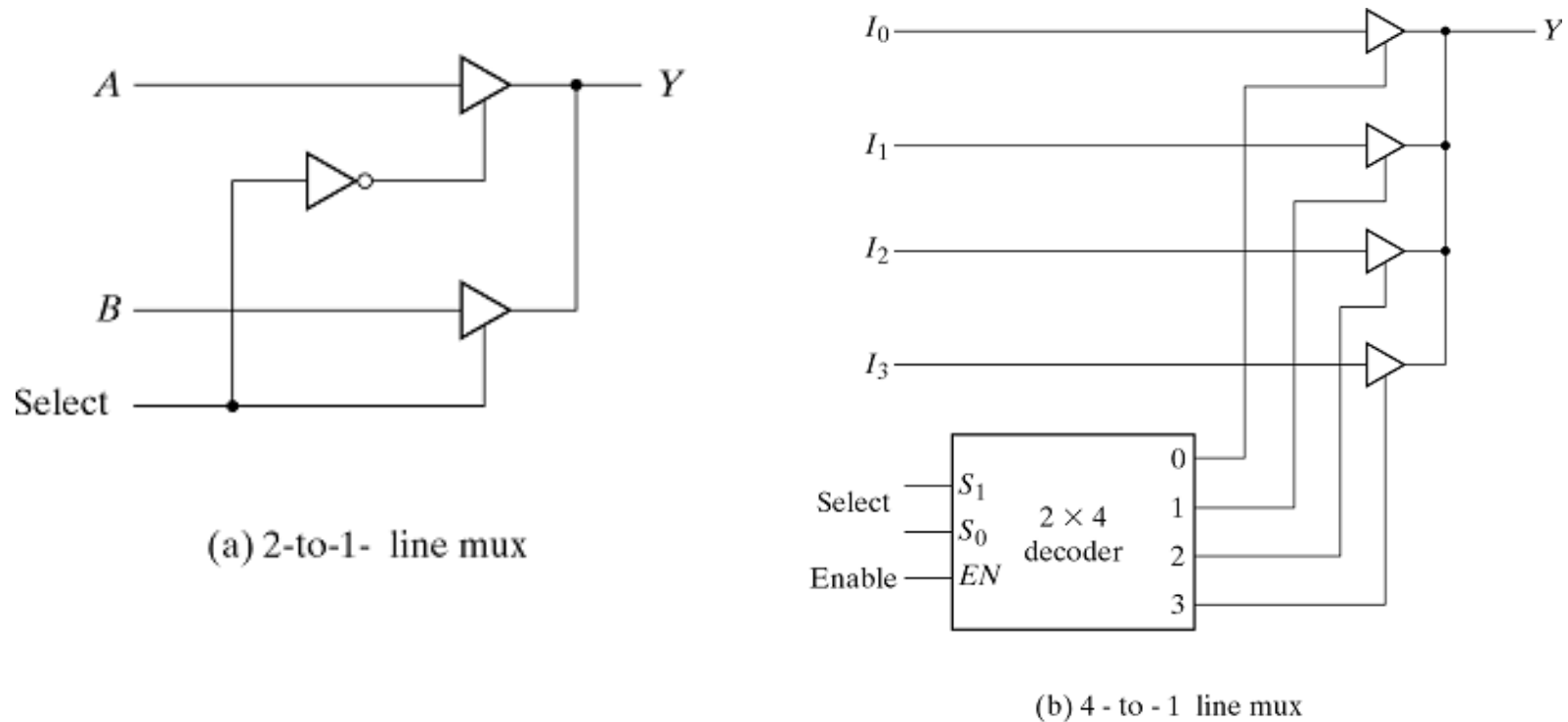


Fig. 4-30 Multiplexers with Three-State Gates